




**COLORADO SCHOOL OF MINES
ELECTRICAL ENGINEERING & COMPUTER SCIENCE DEPARTMENT**

**EENG-382
Engineering Circuit Analysis (Circuits II)
Spring 2014**

Handwritten Homework #2 (HW02)

Problem #1

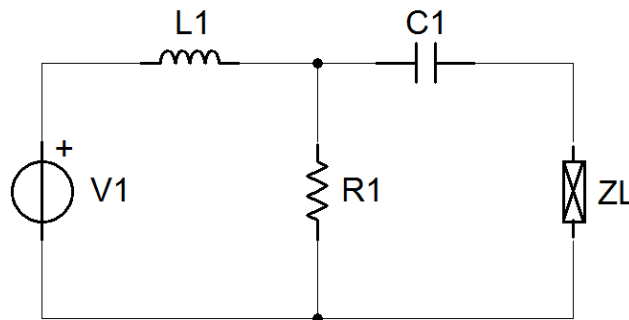

In the above circuit, the voltage source V_1 is $75V_{\text{eff}}$ at a frequency of 400Hz. The other circuit components are $R_1=820\Omega$, $L_1=33\text{mH}$, and $C_1=470\text{nF}$.

- What value of Z_L will result in maximum average power delivered to it?
- What will the complex power delivered to the load in part (a) be?
- What percentage of the real power delivered by the source will be absorbed by the load?
- If the load is to be constructed using just two components from the list of components in Appendix H, draw a circuit for Z_L that will absorb the maximum power.
- What fraction of the maximum average power that could potentially be delivered to the load will be delivered to the circuit in part (d)?