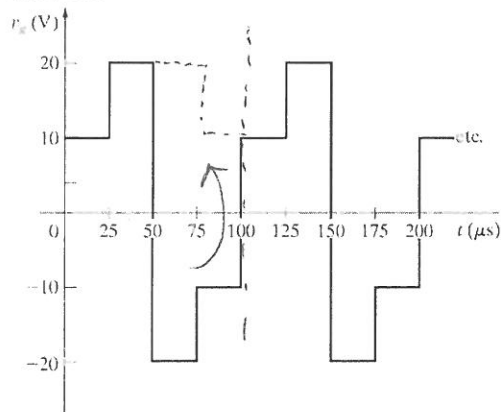


**Problem #1 (12 pts)**

- 10.15 a) Find the rms value of the periodic voltage shown in Fig. P10.15.  
 b) If this voltage is applied to the terminals of a  $4\ \Omega$  resistor, what is the average power dissipated in the resistor?

Figure P10.15



$$V_{RMS}^2 = \frac{1}{2}(10V)^2 + \frac{1}{2}(20V)^2$$

$$V_{RMS}^2 = 50V^2 + 200V^2$$




$$V_{RMS} = \sqrt{250V^2} = 15.81V \leftarrow \text{(#1a)}$$

$$P_{AVG} = \frac{V_{RMS}^2}{R} = \frac{250V^2}{4\Omega} = 62.5W \leftarrow \text{(#1b)}$$

**Problem #2 (16 pts)**

A balanced Y-connected load having an impedance of  $(80+j60) \Omega/\phi$  is connected to a  $\Delta$ -connected source in which each generator is producing 10kV (rms).

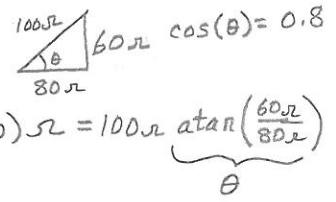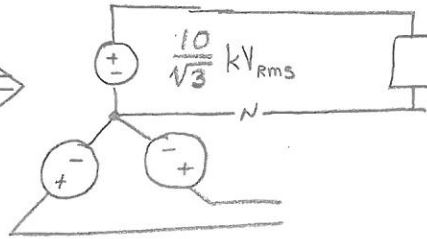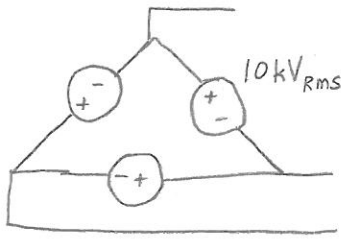- a) What is the apparent power produced by the generator set?
- b) What is the real power consumed by the load?
- c) What is the complex power produced by the generator set?
- b) What is the power factor of the load?



SINGLE PHASE EQUIVALENT

$$\bar{V}_{RMS} = \frac{10}{\sqrt{3}} \text{ kV} \angle -\theta$$

$$\bar{I}_{RMS} = \frac{10 \text{ kV}}{\sqrt{3} \cdot 100 \Omega \angle \theta} = \frac{1}{10\sqrt{3}} \text{ kA} \angle -\theta$$

$$|\bar{S}|_{PH} = V_{RMS} \cdot I_{RMS} = \left(\frac{10}{\sqrt{3}} \text{ kV}\right) \left(\frac{1}{10\sqrt{3}} \text{ kA}\right) = \frac{1}{3} \text{ MVA (PER PHASE)} \quad (2A)$$

$$|\bar{S}|_{TOT} = 3 \cdot |\bar{S}|_{PH} = 3 \cdot \frac{1}{3} \text{ MVA} = 1 \text{ MVA} \leftarrow$$

$$pf = \cos(\theta) = 0.8 \quad (2B)$$

$$P_{AVG} = S \cdot pf = 1 \text{ MVA} \cdot 0.8 \frac{\text{W}}{\text{MVA}} = 800 \text{ kW} \leftarrow$$

$$\bar{S} = |\bar{S}| \angle \theta = |\bar{S}| \cos \theta + j |\bar{S}| \sin(\theta) \quad (2C)$$


$$\bar{S} = 1 \text{ MVA} \cdot 0.8 + j 1 \text{ MVA} \cdot 0.6 = 800 \text{ kW} + j 600 \text{ kW} \leftarrow$$

$$pf = \cos(\theta) = 0.8 \text{ (lagging)} \leftarrow \quad (2D)$$

**Problem #3 (12 pts)**


- 10.44 a) Determine the load impedance for the circuit shown in Fig. P10.44 that will result in maximum average power being transferred to the load if  $\omega = 5 \text{ krad/s}$ .

Figure P10.44

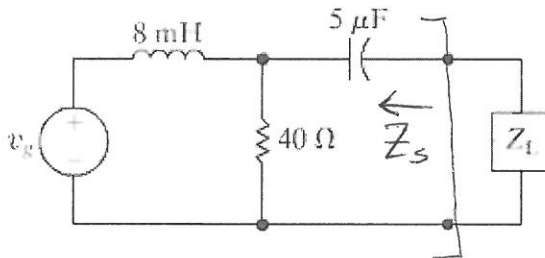

$$5 \mu\text{F} \Rightarrow \frac{1}{j 5 \text{ k} / \text{s} \cdot 5 \mu\text{F}} = -j 40 \Omega$$
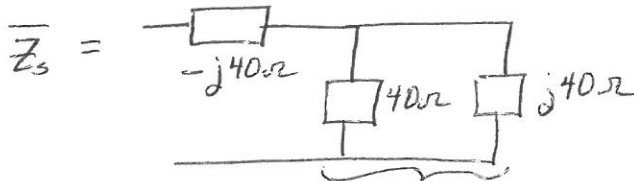
$$8 \text{ mH} \Rightarrow j 5 \text{ k} / \text{s} \cdot 8 \text{ mH} = j 40 \Omega$$



$$\frac{(40 \Omega)(j 40 \Omega)}{(40 \Omega + j 40 \Omega)} = 40 \Omega \frac{j(1-j)}{(1+j)(1-j)} = 20 \Omega (1+j)$$

$$\begin{aligned} \bar{Z}_s &= 20 \Omega (1+j) - j 40 \Omega = 20 \Omega (1+j - j 2) \\ &= 20 \Omega (1-j) \end{aligned}$$

$$\underline{\underline{\bar{Z}_L = \bar{Z}_s^* = 20 \Omega (1+j)}}$$

(#3)

**Problem #4 (10 pts)**

Find the one-sided Laplace transform of the following function beginning with the definition of the one-sided Laplace transform.

$$e^{-at} \sin \omega t$$

(damped sine)

$$\begin{aligned} \mathcal{L}\{e^{-at} \sin(\omega t)\} &= \int_0^{\infty} e^{-at} \sin(\omega t) e^{-st} dt \\ &= \int_0^{\infty} \frac{e^{j\omega t} - e^{-j\omega t}}{2j} e^{-(s+a)t} dt \\ &= \frac{1}{2j} \int_0^{\infty} e^{-(s+a-j\omega)t} - e^{-(s+a+j\omega)t} dt \\ &= \frac{1}{2j} \left[ \frac{-1}{s+a-j\omega} e^{-(s+a-j\omega)t} - \frac{-1}{s+a+j\omega} e^{-(s+a+j\omega)t} \right]_0^{\infty} \\ &= \frac{1}{2j} \left[ \frac{1}{s+a-j\omega} - \frac{1}{s+a+j\omega} \right] \\ &= \frac{1}{2j} \left[ \frac{(s+a+j\omega) - (s+a-j\omega)}{(s+a-j\omega)(s+a+j\omega)} \right] \\ &= \frac{1}{2j} \left[ \frac{2j\omega}{(s+a)^2 + \omega^2} \right] \end{aligned}$$

$$\mathcal{L}\{e^{-at} \sin(\omega t)\} = \frac{\omega}{(s+a)^2 + \omega^2} \quad \leftarrow \text{(#4)}$$

Problem #5 (10 pts)

Prove/derive the following operational Laplace transform.

 $tf(t)$ 

$$-\frac{dF(s)}{ds}$$

$$\begin{aligned}
 F(s) &= \int_{0^-}^{\infty} f(t) e^{-st} dt \\
 \frac{dF(s)}{ds} &= \frac{d}{ds} \int_{0^-}^{\infty} f(t) e^{-st} dt \\
 &= \int_{0^-}^{\infty} \frac{d}{ds} (f(t) e^{-st}) dt \\
 &= \int_{0^-}^{\infty} f(t) \frac{d}{ds} e^{-st} dt \\
 &= \int_{0^-}^{\infty} f(t) (-t) e^{-st} dt \\
 &= - \int_{0^-}^{\infty} t f(t) e^{-st} dt \\
 &= - \mathcal{L} \{ t f(t) \}
 \end{aligned}$$

$$\therefore \mathcal{L} \{ t f(t) \} = - \frac{dF(s)}{ds} \leftarrow (\#5)$$


---