

**Problem #1 (20 pts)**

- 13.64 a) Use the convolution integral to find the output voltage of the circuit in Fig. P13.50(a) if the input voltage is the rectangular pulse shown in Fig. P13.64.
- b) Sketch  $v_o(t)$  versus  $t$  for the time interval  $0 \leq t \leq 10$  ms.

Figure P13.64


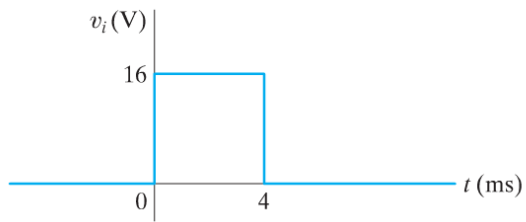


Figure P13.50

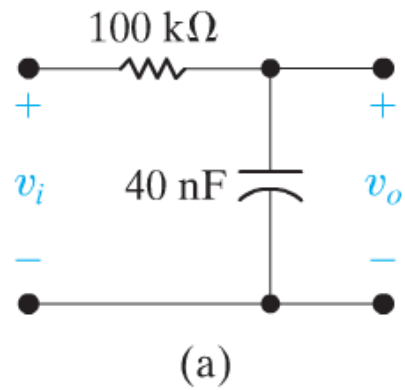


**Problem #2 (20 pts)**

**14.37** Assume the bandreject filter in Problem 14.36 is loaded with a  $1\text{ k}\Omega$  resistor.

PSPICE  
MULTISIM


- What is the quality factor of the loaded circuit?
- What is the bandwidth (in kilohertz) of the loaded circuit?
- What is the upper cutoff frequency in kilohertz?
- What is the lower cutoff frequency in kilohertz?

Figure P14.36

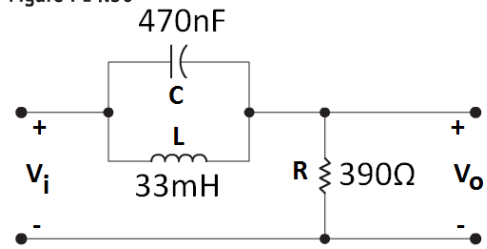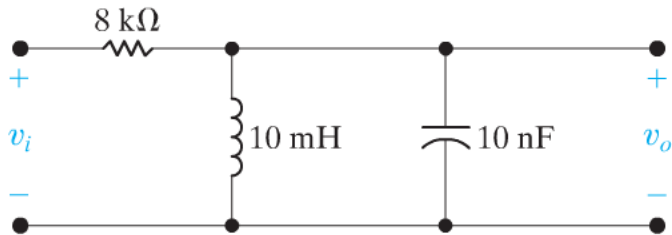

**Problem #3 (20 pts)**

**15.24** Scale the bandpass filter in Problem 14.22 so that the center frequency is 200 kHz and the quality factor is still 8, using a 2.5 nF capacitor. Determine the values of the resistor, the inductor, and the two cut-off frequencies of the scaled filter.

**Figure P14.22**

**TABLE OF LAPLACE TRANSFORMS**

An Abbreviated List of Laplace Transform Pairs		
$f(t) (t > 0^-)$	Type	$F(s)$
$\delta(t)$	(impulse)	1
$u(t)$	(step)	$\frac{1}{s}$
$t$	(ramp)	$\frac{1}{s^2}$
$e^{-at}$	(exponential)	$\frac{1}{s + a}$
$\sin \omega t$	(sine)	$\frac{\omega}{s^2 + \omega^2}$
$\cos \omega t$	(cosine)	$\frac{s}{s^2 + \omega^2}$
$te^{-at}$	(damped ramp)	$\frac{1}{(s + a)^2}$
$e^{-at} \sin \omega t$	(damped sine)	$\frac{\omega}{(s + a)^2 + \omega^2}$
$e^{-at} \cos \omega t$	(damped cosine)	$\frac{s + a}{(s + a)^2 + \omega^2}$

An Abbreviated List of Operational Transforms	
$f(t)$	$F(s)$
$Kf(t)$	$KF(s)$
$f_1(t) + f_2(t) - f_3(t) + \dots$	$F_1(s) + F_2(s) - F_3(s) + \dots$
$\frac{df(t)}{dt}$	$sF(s) - f(0^-)$
$\frac{d^2 f(t)}{dt^2}$	$s^2 F(s) - sf(0^-) - \frac{df(0^-)}{dt}$
$\frac{d^n f(t)}{dt^n}$	$s^n F(s) - s^{n-1} f(0^-) - s^{n-2} \frac{df(0^-)}{dt} - s^{n-3} \frac{d^2 f(0^-)}{dt^2} - \dots - \frac{d^{n-1} f(0^-)}{dt^{n-1}}$
$\int_0^t f(x) dx$	$\frac{F(s)}{s}$
$f(t - a)u(t - a), a > 0$	$e^{-as} F(s)$
$e^{-at} f(t)$	$F(s + a)$
$f(at), a > 0$	$\frac{1}{a} F\left(\frac{s}{a}\right)$
$tf(t)$	$-\frac{dF(s)}{ds}$
$t^n f(t)$	$(-1)^n \frac{d^n F(s)}{ds^n}$
$\frac{f(t)}{t}$	$\int_s^\infty F(u) du$

Filter Type	Transfer Function
Low Pass	$H(s) = \frac{\omega_c}{s + \omega_c}$
High Pass	$H(s) = \frac{s}{s + \omega_c}$
Band Pass	$H(s) = \frac{\beta s}{s^2 + \beta s + \omega_0^2}$
Band Reject	$H(s) = \frac{s^2 + \omega_0^2}{s^2 + \beta s + \omega_0^2}$
Resistor Scaling	$R' = k_m R$
Inductor Scaling	$L' = \frac{k_m}{k_f} L$
Capacitor Scaling	$C' = \frac{1}{k_m k_f} C$