

EENG382 HW02 – AUTHOR'S SOLUTIONS

NOTE: I have not yet verified that the author's solutions are, in fact, correct.

Prob 10.29

$$\text{P 10.29 [a] } \mathbf{I} = \frac{465/0^\circ}{124 + j93} = 2.4 - j1.8 = 3/\underline{-36.87^\circ} \text{ A(rms)}$$

$$P = (3)^2(4) = 36 \text{ W}$$

$$\text{[b] } Y_L = \frac{1}{120 + j90} = 5.33 - j4 \text{ mS}$$

$$\therefore X_C = \frac{1}{-4 \times 10^{-3}} = -250 \Omega$$

$$\text{[c] } Z_L = \frac{1}{5.33 \times 10^{-3}} = 187.5 \Omega$$

$$\text{[d] } \mathbf{I} = \frac{465/0^\circ}{191.5 + j3} = 2.4279/\underline{-0.9^\circ} \text{ A}$$

$$P = (2.4279)^2(4) = 23.58 \text{ W}$$

$$\text{[e] } \% = \frac{23.58}{36}(100) = 65.5\%$$


Thus the power loss after the capacitor is added is 65.5% of the power loss before the capacitor is added.

Prob 10.49

P 10.49 [a] $Z_{Th} = 20 + j60 + \frac{(j20)(6 - j18)}{6 + j2} = 80 + j60 = 100\angle 36.87^\circ \Omega$

$\therefore R = |Z_{Th}| = 100 \Omega$

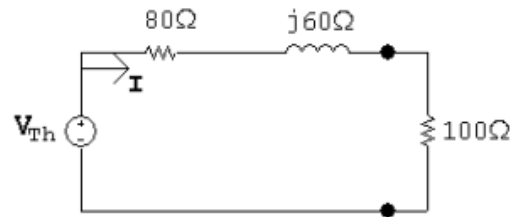[b] $V_{Th} = \frac{j20}{6 - j18 + j20}(480\angle 0^\circ) = 480 + j1440 \text{ V(rms)}$



$I = \frac{480 + j1440}{180 + j60} = 4.8 + j6.4 = 8\angle 53.13^\circ \text{ A(rms)}$

$P = 8^2(100) = 6400 \text{ W}$

[c] Pick the 100 Ω resistor from Appendix H to match exactly.

Prob 10.69

$$\text{P 10.69 } R_1 + R_2 + R_3 = \frac{(120)^2}{600} = 24 \Omega$$

$$R_2 + R_3 = \frac{(120)^2}{900} = 16 \Omega$$

$$\therefore R_1 = 24 - 16 = 8 \Omega$$

$$R_3 + R_1 \parallel R_2 = \frac{(120)^2}{1200} = 12 \Omega$$

$$\therefore 16 - R_2 + \frac{8R_2}{8 + R_2} = 12$$

$$R_2 - \frac{8R_2}{8 + R_2} = 4$$

$$8R_2 + R_2^2 - 8R_2 = 32 + 4R_2$$

$$R_2^2 - 4R_2 - 32 = 0$$

$$R_2 = 2 \pm \sqrt{4 + 32} = 2 \pm 6$$

$$\therefore R_2 = 8 \Omega; \quad \therefore R_3 = 8 \Omega$$