




COLORADO SCHOOL OF MINES  
ELECTRICAL ENGINEERING & COMPUTER SCIENCE DEPARTMENT

EENG-382  
Engineering Circuit Analysis (Circuits II)  
Spring 2014

Handwritten Homework #1 (HW01)

**Problem #1**

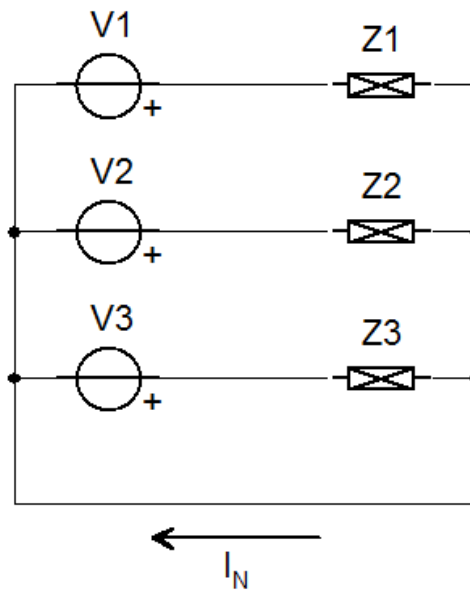

- If each voltage source is independent (i.e., has its own magnitude and phase) and each impedance is independent, find an expression for the phasor current  $\mathbf{I}_N$  in the bottom wire?
- If  $\mathbf{V}_1 = 120\text{V}\angle 35^\circ$ ,  $\mathbf{V}_2 = 100\text{V}\angle -55^\circ$ ,  $\mathbf{V}_3 = 150\text{V}\angle 165^\circ$  and  $\mathbf{Z}_1 = (40+j70)\Omega$ ,  $\mathbf{Z}_2 = (20-j35)\Omega$ ,  $\mathbf{Z}_3 = 60\Omega\angle 50^\circ$ , what is  $\mathbf{I}_N$ ?
- If all three impedances are equal to  $\mathbf{Z}$ , what is the constraint that applies to the three voltages in order for  $\mathbf{I}_N$  to be identically zero?
- If, in addition to all three impedances being equal, all three voltage sources have the same magnitude, what is the constraint that applies to the three phase angles in order for  $\mathbf{I}_N$  to be identically zero.