

Problem #1 (20 pts)

- 13.64 a) Use the convolution integral to find the output voltage of the circuit in Fig. P13.50(a) if the input voltage is the rectangular pulse shown in Fig. P13.64.
 b) Sketch $v_o(t)$ versus t for the time interval $0 \leq t \leq 10$ ms.


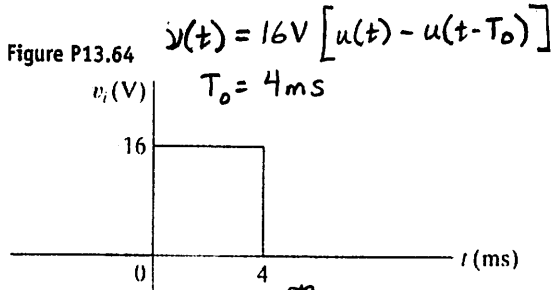


Figure P13.50

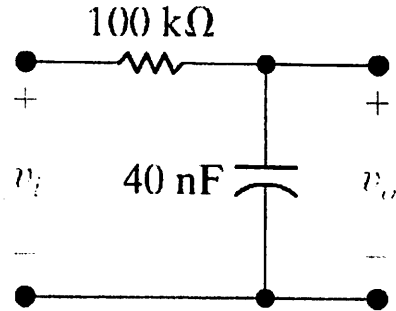

$$v_o(t) = v_i(t) * h(t) = \int_{-\infty}^{\infty} v_i(\lambda) h(t-\lambda) d\lambda$$

$$h(t-\lambda) = \frac{1}{\tau} e^{-\frac{(t-\lambda)}{\tau}} u(t-\lambda) = \frac{1}{\tau} e^{-\frac{t-\lambda}{\tau}} e^{\frac{\lambda}{\tau}} u(t-\lambda)$$

$$v_o(t) = \int_{-\infty}^{\infty} 16V [u(\lambda) - u(\lambda - T_0)] \frac{1}{\tau} e^{-\frac{t-\lambda}{\tau}} e^{\frac{\lambda}{\tau}} u(t-\lambda) d\lambda$$

$$= \frac{16V}{\tau} e^{-\frac{t}{\tau}} \left[\int_{-\infty}^{\infty} e^{\frac{\lambda}{\tau}} u(\lambda) u(t-\lambda) d\lambda - \int_{-\infty}^{\infty} e^{\frac{\lambda}{\tau}} u(\lambda - T_0) u(t-\lambda) d\lambda \right]$$

$$= \frac{16V}{\tau} e^{-\frac{t}{\tau}} \left[\int_0^t e^{\frac{\lambda}{\tau}} d\lambda - \int_{T_0}^{t-T_0} e^{\frac{\lambda}{\tau}} d\lambda \right]$$

(a)

$$H(s) = \frac{Z_c}{R + Z_c} = \frac{\frac{1}{sC}}{R + \frac{1}{sC}} = \frac{1}{sRC + 1}$$

$$H(s) = \frac{1}{RC} \cdot \frac{1}{s + \frac{1}{RC}} = \frac{1}{\tau} \cdot \frac{1}{s + 1/\tau}$$

$$\tau = RC = (100k\Omega)(40nF) = 4ms$$

$$h(t) = \mathcal{L}^{-1}\{H(s)\}$$

$$= \frac{1}{\tau} \mathcal{L}^{-1}\left\{\frac{1}{s + 1/\tau}\right\}$$

$$h(t) = \frac{1}{\tau} e^{-\frac{t}{\tau}} u(t)$$

FOR $0 \leq t \leq T_0$

$$v_o(t) = \frac{16V}{\tau} e^{-\frac{t}{\tau}} \int_0^t e^{\frac{\lambda}{\tau}} d\lambda = \frac{16V}{\tau} e^{-\frac{t}{\tau}} \cdot \tau e^{\frac{\lambda}{\tau}} \Big|_0^t = 16V e^{-\frac{t}{\tau}} (e^{\frac{t}{\tau}} - 1)$$

$$v_o(t) = 16V (1 - e^{-\frac{t}{\tau}}) = 16V (1 - e^{-\frac{t}{4ms}})$$

FOR $T_0 \leq t$

$$v_o(t) = \frac{16V}{\tau} e^{-\frac{t}{\tau}} \int_0^{T_0} e^{\frac{\lambda}{\tau}} d\lambda = \frac{16V}{\tau} e^{-\frac{t}{\tau}} \tau e^{\frac{\lambda}{\tau}} \Big|_0^{T_0} = 16V e^{-\frac{t}{\tau}} (e^{\frac{T_0}{\tau}} - 1) = 16V$$


$$v_o(t) = 16V (e^{\frac{4ms}{4ms}} - 1) e^{-\frac{t}{4ms}} = 16(e-1)V e^{-\frac{t}{4ms}} = 27.49V e^{-\frac{t}{4ms}}$$

$$v_o(t) = \begin{cases} 0V & t < 0 \\ 16V (1 - e^{-\frac{t}{4ms}}) & 0 \leq t \leq 4ms \\ 27.5V e^{-\frac{t}{4ms}} & 4ms < t \end{cases}$$

$$v_o(4ms) = 16V \cdot (1 - e^{-1}) = 10.11V$$

$$v_o(4ms) = 27.49V e^{-1} = 10.11V$$

AGREE ✓

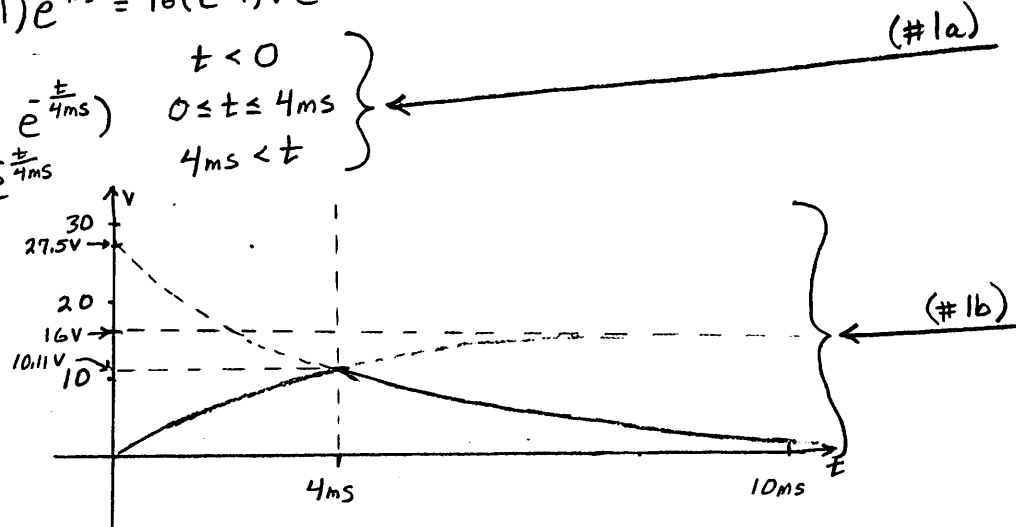


Problem #2 (20 pts)

14.37 Assume the bandreject filter in Problem 14.36 is loaded with a 1 kΩ resistor.

PSRU
MUESM

- a) What is the quality factor of the loaded circuit?
- b) What is the bandwidth (in kilohertz) of the loaded circuit?
- c) What is the upper cutoff frequency in kilohertz?
- d) What is the lower cutoff frequency in kilohertz?

Figure P14.36

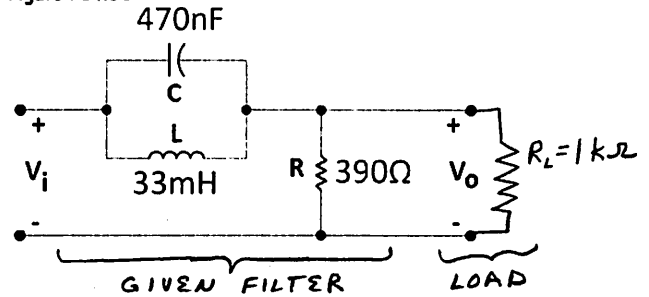

$$R' = (R || R_L) = \frac{(390\Omega)(1000\Omega)}{(1390\Omega)} = 280.6\Omega$$

$$H(s) = \frac{V_o}{V_i} = \frac{R'}{R' + (Z_L || Z_C)} = \frac{R'}{R' + \frac{Z_L Z_C}{Z_L + Z_C}} = \frac{R'(Z_L + Z_C)}{R'(Z_L + Z_C) + Z_L Z_C}$$

$$= \frac{R'(sL + \frac{1}{sC})}{R'(sL + \frac{1}{sC}) + (sL)(\frac{1}{sC})} = \frac{(R'Ls + \frac{R'}{sC})}{(R'Ls + \frac{L}{C} + \frac{1}{s} \cdot \frac{R'}{C})} \cdot \left(\frac{s}{R'L}\right)$$

$$H(s) = \frac{(s^2 + \frac{1}{LC})}{(s^2 + \frac{1}{R'C}s + \frac{1}{LC})} \Rightarrow s^2 + \beta s + \omega_0^2$$

$$Q = \frac{\omega_0}{\beta} = \frac{\sqrt{\frac{1}{LC}}}{\frac{1}{R'C}} = \frac{R'C}{\sqrt{LC}} = \sqrt{\frac{R'^2 C^2}{LC}} = R' \sqrt{\frac{C}{L}} = 280.6\Omega \sqrt{\frac{470nF}{33mH}}$$

$$= 280.6\Omega \sqrt{\frac{470nF}{33mH}} = 280.6\Omega \sqrt{\frac{470n \frac{sec}{\Omega}}{33m \frac{\Omega}{sec}}} = 280.6\Omega \cdot \sqrt{\frac{470}{33} \mu \left(\frac{1}{\Omega^2}\right)}$$

(#2a)

Q = 1.059 ←

$$\beta = \frac{1}{R'C} = \frac{1}{280.6\Omega \cdot 470n \frac{sec}{\Omega}} \cdot \frac{1Hz}{2\pi \cdot 1/2\pi} = 1209.4 Hz$$

(#2b)

β = 1.209 kHz ←

$$f_{c1} f_{c2} = f_0^2; f_{c1} = f_{c2} - \beta = f_{c2} - \frac{f_0}{Q}; (f_{c2} - \frac{f_0}{Q}) f_{c2} = f_0^2$$

$$f_{c2}^2 - \frac{f_0}{Q} f_{c2} - f_0^2 = 0$$

$$f_{c2} = \frac{1}{2} \left(\frac{f_0}{Q} \pm \sqrt{\left(\frac{f_0}{Q}\right)^2 + 4f_0^2} \right) = f_0 \left(\frac{1}{2Q} \pm \sqrt{\left(\frac{1}{2Q}\right)^2 + 1} \right) = \frac{1}{\sqrt{LC}} \left(\frac{1}{2Q} \pm \sqrt{\left(\frac{1}{2Q}\right)^2 + 1} \right)$$

$$f_{c2} = \frac{1}{\sqrt{33mH \cdot 470nF}} \cdot \frac{1Hz}{2\pi \cdot 1s} \cdot \left(\frac{1}{2 \cdot 1.059} \pm \sqrt{\left(\frac{1}{2 \cdot 1.059}\right)^2 + 1} \right) = \frac{1.2780 kHz \cdot 1.5780}{f_0}$$

(#2c)

f_{c2} = 2.02 kHz ←

$$f_{c1} = f_{c2} - \beta = 2.02 kHz - 1.209 kHz = 0.807 kHz$$

(#2d)


f_{c1} = 0.807 kHz ←

CHECK: $f_0 \stackrel{?}{=} \sqrt{f_{c1} f_{c2}} = \sqrt{2.02 kHz \cdot 0.807 kHz} = 1.277 kHz \checkmark$

Problem #3 (20 pts)

15.24 Scale the bandpass filter in Problem 14.22 so that the center frequency is 200 kHz and the quality factor is still 8, using a 2.5 nF capacitor. Determine the values of the resistor, the inductor, and the two cut-off frequencies of the scaled filter.

Figure P14.22

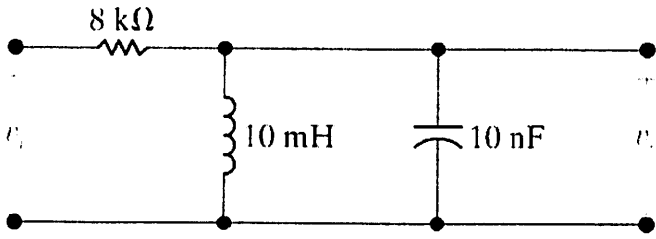

ORIGINAL FILTER: $\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10\text{mH} \cdot 10\text{nF}}} = \frac{1}{\sqrt{100\text{ p}(s^2)}} = \frac{1}{10\mu\text{s}} = 100\text{ kr/s}$

$f_0 = 100\text{ kr/s} \cdot \frac{1\text{ cycle}}{2\pi\text{ rad}} \cdot \frac{1\text{ Hz}}{1\text{ cycle/s}} = 15.916\text{ kHz}$

$\beta = \frac{f_0}{Q} = \frac{15.916\text{ kHz}}{8} = 1.9894\text{ kHz}$

$f_0 = \sqrt{f_{c1} f_{c2}} ; f_{c2} - f_{c1} = \beta = \frac{f_0}{Q}$

$f_0^2 = f_{c1} f_{c2} = f_{c1} (f_{c1} + \frac{f_0}{Q})$

$f_{c1}^2 + \frac{f_0}{Q} f_{c1} - f_0^2 = 0$

$f_{c1} = \left(\frac{-\frac{f_0}{Q} \pm \sqrt{\left(\frac{f_0}{Q}\right)^2 + 4f_0^2}}{2} \right)^{\frac{1}{2}} = \frac{-f_0}{2Q} \pm f_0 \sqrt{\frac{1}{4Q^2} + 1}$

$f_{c1} = f_0 \left(\sqrt{\frac{1}{4Q^2} + 1} - \frac{1}{2Q} \right) = 15.916\text{ kHz} \cdot \left(\sqrt{\frac{1}{4 \cdot 8^2} + 1} - \frac{1}{2 \cdot 8} \right) = 15.916\text{ kHz} \cdot \underline{94.14\%}$

SCALING FACTORS: $k_f = \frac{f_0'}{f_0} = \frac{200\text{ kHz}}{15.916\text{ kHz}} = \underline{12.566}$

$C' = \frac{1}{k_f k_m} C \Rightarrow k_m = \frac{1}{k_f} \cdot \frac{C}{C'} = \frac{1}{12.566} \cdot \frac{10\text{ nF}}{2.5\text{ nF}} = \underline{0.3183}$

SCALED COMPONENTS: $R' = k_m R = 0.3183 \cdot 8\text{ k}\Omega = \underline{2.546\text{ k}\Omega}$

$L' = \frac{k_m}{k_f} L = \frac{0.3183}{12.566} \cdot 10\text{ mH} = \underline{253.3\mu\text{H}}$

NEW FILTER:

$\omega_0' = \frac{1}{\sqrt{L'C'}} = \frac{1}{\sqrt{0.2533\text{ mH} \cdot 2.5\text{ nF}}} \cdot \frac{1\text{ Hz}}{2\pi\text{ r/s}} = 200\text{ kHz} \checkmark$

$f_{c1}' = f_0' \cdot 94.14\% = 200\text{ kHz} \cdot 94.14\% = \underline{188.28\text{ kHz}}$

$f_{c2}' = f_{c1}' + \beta' = f_{c1}' + \frac{f_0'}{Q} = 188.28\text{ kHz} + \frac{200\text{ kHz}}{8} = \underline{213.28\text{ kHz}}$

ANSWERS:

$R' = 2.55\text{ k}\Omega$
 $L' = 253\mu\text{H}$
 $f_{c1}' = 188.3\text{ kHz}$
 $f_{c2}' = 213\text{ kHz}$

(#3)