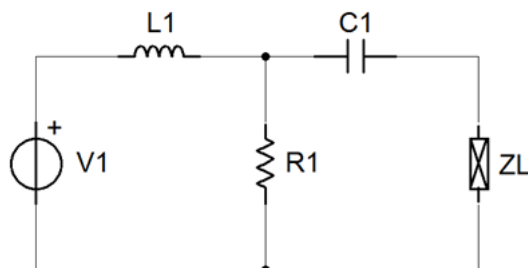


PROBLEM #1



In the above circuit, the voltage source V_1 is $75V_{\text{eff}}$ at a frequency of 400Hz . The other circuit components are $R_1=820\Omega$, $L_1=33\text{mH}$, and $C_1=470\text{nF}$.

- What value of Z_L will result in maximum average power delivered to it?
- What will the complex power delivered to the load in part (a) be?
- What percentage of the real power delivered by the source will be absorbed by the load?
- If the load is to be constructed using just two components from the list of components in Appendix H, draw a circuit for Z_L that will absorb the maximum power.
- What fraction of the maximum average power that could potentially be delivered to the load will be delivered to the circuit in part (d)?

A PYTHON SCRIPT WAS WRITTEN TO PERFORM THE NUMERICAL COMPUTATIONS TO SAVE EFFORT AND REDUCE ERRORS. BOTH THE HOMEWORK SPECIFIC SCRIPT, HW02.PY, AND THE SCRIPT THAT DEFINES GENERIC FUNCTIONS, Z.PY, ARE ATTACHED.

THE OUTPUT OF THE SCRIPT FOLLOWS THE WORK AND IS CROSS-REFERENCED TO THE WORK FOR EASY REFERENCE.

PART (a)

FOR MAX. POWER TRANSFER, WANT

$$\bar{Z}_{\text{LOAD}} = \bar{Z}_{\text{TH}}^*$$

$$\bar{Z}_{\text{TH}} = \bar{Z}_{C_1} + (\bar{Z}_{R_1} \parallel \bar{Z}_{L_1}) \quad (\text{BY INSPECTION})$$

$$\textcircled{1} \quad = 8.30\Omega - j765\Omega$$

$$\bar{Z}_{\text{LOAD}} = 8.30\Omega + j765\Omega \quad \leftarrow \quad (\#1a)$$

PROBLEM #1 (CONT'D)

PART (b)

$$P_{LOAD} = \text{Re} \{ \bar{V}_{LOAD} \cdot \bar{I}_{LOAD}^* \}$$

$$\bar{V}_{LOAD} = \frac{\bar{V}_{TH} \cdot \bar{Z}_{LOAD}}{(\bar{Z}_{TH} + \bar{Z}_{LOAD})}$$

$$\bar{I}_{LOAD}^* = \frac{\bar{V}_{TH}^*}{(\bar{Z}_{TH} + \bar{Z}_{LOAD})^*}$$

$$\begin{aligned} \bar{S}_{LOAD} &= \bar{V}_{LOAD} \cdot \bar{I}_{LOAD} \\ &= \frac{(\bar{V}_{TH} \cdot \bar{V}_{TH}^*) \bar{Z}_{LOAD}}{(\bar{Z}_{TH} + \bar{Z}_{LOAD})(\bar{Z}_{TH} + \bar{Z}_{LOAD})^*} = \frac{|\bar{V}_{TH}|^2}{|\bar{Z}_{TH} + \bar{Z}_{LOAD}|^2} \cdot \bar{Z}_{LOAD} \end{aligned}$$

$$\text{IF } \bar{Z}_{LOAD} = \bar{Z}_{TH}^*$$

$$\bar{Z}_{TH} + \bar{Z}_{LOAD} = R_{TH} + jX_{TH} + R_{TH} - jX_{TH} = 2R_{TH}$$

$$\bar{S}_{LOAD} = \frac{V_{TH}^2}{(2R_{TH})^2} \cdot (R_{TH} - jX_{TH})$$

$$\textcircled{2} \quad \underline{\underline{\bar{S}_{LOAD} = (167.6 + j1543) \text{ VA}}} \quad \leftarrow \quad \text{(#1b)}$$

PART (c)

$$P_{LOAD} = \text{Re} \{ \bar{S}_{LOAD} \} = 167.6 \text{ W}$$

$$P_{SOURCE} = \text{Re} \{ \bar{S}_{SOURCE} \}$$

$$\bar{S}_{SOURCE} = \bar{V}_{SOURCE} \cdot \bar{I}_{SOURCE}^*$$

$$\bar{I}_{SOURCE} = \frac{\bar{V}_{SOURCE}}{\bar{Z}_{TOT}}$$

$$\bar{Z}_{TOT} = \bar{Z}_{L1} + (\bar{Z}_{R1} \parallel (\bar{Z}_{C1} + \bar{Z}_{L2})) \quad (\text{BY INSPECTION})$$

$$\textcircled{3} \quad \bar{Z}_{TOT} = (16.12 + j3.26) \Omega$$

$$\textcircled{4} \quad \bar{S}_{SOURCE} = (335 + j67.8) \text{ VA}$$

$$P_{SOURCE} = \text{Re} \{ \bar{S}_{SOURCE} \} = 335 \text{ W}$$

$$\text{POWER TRANSFER} = \frac{P_{LOAD}}{P_{SOURCE}} = \frac{167.6 \text{ W}}{335 \text{ W}}$$

$$\underline{\underline{\text{POWER TRANSFER} = 50.0\%}} \quad \leftarrow \quad \text{(#1c)}$$

NOTE: YOU CANNOT USE V_{TH} FOR THIS, BUT MUST USE THE ORIGINAL CIRCUIT.


PROBLEM #1 (CONT'D)PART (d)

THE OPTIMAL LOAD IS $\bar{Z}_{LOAD} = 8.30\Omega + j765\Omega = R_{TH} + jX_{TH}$

$$\textcircled{5} R = 8.30\Omega \quad L = \frac{1}{2\pi f X_{TH}} = 304\text{mH} \quad \textcircled{6}$$


THE SMALLEST AVAILABLE RESISTOR IS 10Ω WHILE
THE LARGEST AVAILABLE INDUCTOR IS 10mH .

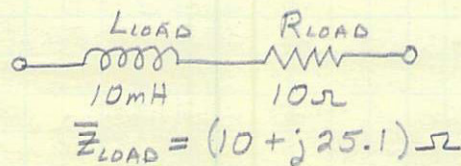A NAIVE ATTEMPT WOULD USE THE COMPONENTS AS
BEING THE CLOSEST MATCH, YIELDING THE FOLLOWING
LOAD:



HOWEVER, THE PROPER METHOD IS TO CHOOSE X_{LOAD}
SO AS TO OFFSET AS MUCH OF X_{TH} AS POSSIBLE AND
THE SET R_{LOAD} EQUAL TO THE MAGNITUDE OF THE
REST OF THE EFFECTIVE COMPONENT'S IMPEDANCE.

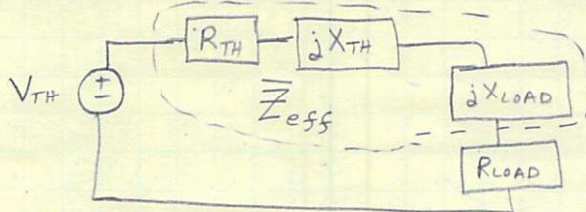THIS PROCESS IS OUTLINED IN THE TEXT (SEC 10.6-p388)




$$R_{LOAD} = |\bar{Z}_{eff}| = |Z_{TH} + jX_{LOAD}|$$

$$= \sqrt{R_{TH}^2 + (X_{TH} + X_{LOAD})^2}$$

$$\textcircled{7} R_{LOAD} = 739\Omega \quad (\text{CHOICE OF } 680\Omega \text{ OR } 1000\Omega)$$

$$\checkmark 680\Omega \text{ IS } \frac{(680\Omega - 739\Omega)}{739\Omega} = \frac{-59}{739} = 8.0\% \text{ TOO SMALL}$$
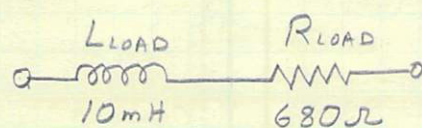
$$1000\Omega \text{ IS } \frac{(1000\Omega - 739\Omega)}{739\Omega} = \frac{261}{739} = 35.3\% \text{ TOO BIG}$$



$$\bar{Z}_{LOAD} = (680 + j25.1)\Omega$$

(#1d)

PROBLEM #1 (CONT'D)PART (e)

THE MAXIMUM POTENTIAL POWER THAT COULD BE DELIVERED TO THE LOAD IS WHEN THE OPTIMAL LOAD, \bar{Z}_{TH}^* , IS USED. THUS, P_{MAX} IS THE RESULT GIVEN IN PARTS (b) & (c).

$$P_{MAX} = 167.6 \text{ W}$$

THE THEVENIN EQUIVALENT CIRCUIT IN PART (b) CAN BE USED WITH THE NON-IDEAL LOAD AND THE P_{AVG} THAT RESULTS CAN BE DIVIDED BY P_{MAX} ABOVE.

$$P_{AVG} = \text{Re} \{ \bar{S}_{LOAD} \}$$

$$= \text{Re} \{ \bar{V}_{LOAD} \bar{I}_{LOAD}^* \}$$

$$P_{AVG} = \text{Re} \{ (\bar{I}_{LOAD} \cdot \bar{Z}_{LOAD}) \bar{I}_{LOAD}^* \}$$

$$\left(\bar{I}_{LOAD} = \frac{\bar{V}_{TH}}{\bar{Z}_{TH} + \bar{Z}_{LOAD}} \right)$$

FOR THE NAIVE ATTEMPT ($R_{LOAD} = 10 \Omega$), THE RESULT IS

$$\textcircled{8} \left\{ \begin{array}{l} \bar{S}_{LOAD} = (101.8 + j256) \text{ mVA} \\ P_{AVG} = 0.0607\% \text{ OF } P_{MAX} \end{array} \right.$$

FOR THE BEST AVAILABLE LOAD ($R_{LOAD} = 680 \Omega$):

$$\textcircled{9} \left\{ \begin{array}{l} \bar{S}_{LOAD} = (3.711 + j0.137) \text{ VA} \\ P_{AVG} = 2.21\% \text{ OF } P_{MAX} \end{array} \right. \leftarrow \text{(#1e)}$$

FOR COMPLETENESS, THE RESULTS WERE ALSO RUN FOR 739 Ω AND 1000 Ω :

R_{LOAD}	P_{AVG}	% P_{MAX}
739 Ω	3.724 W	2.22%
1000 Ω	3.562 W	2.12%

THUS, THE 680 Ω IS CLEARLY THE BETTER CHOICE AND IS VERY CLOSE THE THE BEST PERFORMANCE WITH THE 10mH CONSTRAINT. ALSO, NOTE THAT IT ABSORBS MORE THAN 36X THE POWER AS WOULD THE 10 Ω RESISTOR.

Output from HW02.py script:

Thevenin Equivalent Circuit

$V_{th} = 74.24 - 7.509j \text{ V} = (74.62 \text{ @ } -5.775 \text{ deg V})$

① $Z_{th} = 8.304 - 764.5j \text{ ohms}$

Optimal load for max power transfer

$Z \text{ load} = 8.304 + 764.5j \text{ ohms}$

⑤ $R \text{ opt} = 8.3 \text{ ohms}$

⑥ $L \text{ opt} = 0.304 \text{ H}$

Power transfer with optimal load

③ $Z \text{ total} = 16.12 + 3.26j \text{ ohms (seen by source)}$

$I \text{ source} = 4.47 - 0.9043j \text{ A} = (4.561 \text{ @ } -11.44 \text{ deg A})$

④ $S \text{ source} = 335.3 + 67.82j \text{ VA} = (342.1 \text{ @ } 11.44 \text{ deg VA})$

$I \text{ load} = 4.47 - 0.4521j \text{ A} = (4.493 \text{ @ } -5.775 \text{ deg A})$

$V \text{ load} = 382.8 + 3414j \text{ V} = (3435 \text{ @ } 83.6 \text{ deg V})$

② $S \text{ load} = 167.6 + 1.543e+04j \text{ VA} = (1.543e+04 \text{ @ } 89.38 \text{ deg VA})$

$P \text{ load} = 50\% \text{ of } P \text{ source}$

Constrained load -- match R as close as possible

$Z \text{ load} = 10 + 25.13j \text{ ohms}$

$I \text{ load} = 0.01263 + 0.1001j \text{ A} = (0.1009 \text{ @ } 82.81 \text{ deg A})$

$V \text{ load} = -2.389 + 1.319j \text{ V} = (2.729 \text{ @ } 151.1 \text{ deg V})$

⑧ $S \text{ load} = 0.1018 + 0.2559j \text{ VA} = (0.2754 \text{ @ } 68.3 \text{ deg VA})$

$P \text{ load} = 0.0607\% \text{ of potential load power}$

Constrained load -- match $-X_{th}$ as close as possible

⑦ $R \text{ ideal} = 739 \text{ ohm}$

$Z \text{ load} = 680 + 25.13j \text{ ohms}$

$I \text{ load} = 0.05552 + 0.04873j \text{ A} = (0.07387 \text{ @ } 41.27 \text{ deg A})$

$V \text{ load} = 36.53 + 34.53j \text{ V} = (50.27 \text{ @ } 43.39 \text{ deg V})$

⑨ $S \text{ load} = 3.711 + 0.1371j \text{ VA} = (3.713 \text{ @ } 2.117 \text{ deg VA})$

$P \text{ load} = 2.21\% \text{ of potential load power}$

```

#=====
# USERID:.....wbahn
# PROGRAMMER:.....Bahn, William L.
# COURSE:.....EENG-382
# TERM:.....SP14
# PROJECT:.....N/A
# FILENAME:.....HW02.py
# PYTHON VERSION:..3.3.3
#=====

```

```
from z import *
```

```

Vs = 75 # 75 Vrms
R1 = 820 # 820 ohms
L1 = 0.033 # 33mH
C1 = 470e-9 # 470nF
freq = 400 # 400 Hz

```

```
# Compute phasors and impedances
```

```

VS = ZR(Vs)
ZR1 = ZR(R1)
ZL1 = ZL(L1, freq)
ZC1 = ZC(C1, freq)

```

```
# Compute Thevenin equivalent circuit ①
```

```

print()
print("Thevenin Equivalent Circuit")
Vth = VS*ZR1/(ZL1+ZR1)
Zth = s(ZC1, p(ZR1, ZL1))
print("Vth = %s V = (%s V)" % (showR(Vth), showP(Vth)))
print("Zth = %s ohms" % showR(Zth))

```

```
# Optimal Load ⑤ ⑥
```

```

print()
print("Optimal load for max power transfer")
Zload = Zstar(Zth)
print("Z load = %s ohms" % showR(Zload))
print("R opt = %3.3g ohms" % R(Zload))
if (X(Zload)<0):
    print("C opt = %3.3g F" % C(X(Zload), freq))
else:
    print("L opt = %3.3g H" % L(X(Zload), freq))

```

```
# Compute total impedance seen by source ③
```

```

print()
print("Power transfer with optimal load")
Zeq = s(ZL1, p(ZR1, s(ZC1, Zload)))
print("Z total = %s ohms (seen by source)" % showR(Zeq))

```

```
# Compute source parameters ④
```

```

IS = VS/Zeq
print("I source = %s A = (%s A)" % (showR(IS), showP(IS)))

```

```
SS = VS*Zstar(IS)
```

```

print ("S source = %s VA = (%s VA)" % (showR(SS), showP(SS)))

# Compute load parameters ②
IL = Vth/(Zth+Zload)
print ("I load = %s A = (%s A)" % (showR(IL), showP(IL)))
.
VL = IL*Zload
print ("V load = %s V = (%s V)" % (showR(VL), showP(VL)))

SL = VL*Zstar(IL)
print ("S load = %s VA = (%s VA)" % (showR(SL), showP(SL)))

# Compute fraction of source power delivered to load
Psource = P(SS)
Pmax = P(SL)
print ("P load = %3.3g%% of P source" % (100*(Pmax/Psource)))

# Constrained component values attempt #1 -- match R
print ()
print ("Constrained load -- match R as close as possible")
R_s = 10 # 10 ohm (smallest available R)
L_s = 0.01 # 10 mH (largest available L)

Zload = ZR(R_s)+ZL(L_s, freq)
print ("Z load = %s ohms" % showR(Zload))

# Compute load parameters ⑧
IL = Vth/(Zth+Zload)
print ("I load = %s A = (%s A)" % (showR(IL), showP(IL)))
.
VL = IL*Zload
print ("V load = %s V = (%s V)" % (showR(VL), showP(VL)))

SL = VL*Zstar(IL)
print ("S load = %s VA = (%s VA)" % (showR(SL), showP(SL)))

# Compute fraction of source power delivered to load
Pload = P(SL)
print ("P load = %3.3g%% of potential load power" % (100*(Pload/Pmax)))

# Constrained component values attempt #1 -- match -X
print ()
print ("Constrained load -- match -Xth as close as possible")
L_s = 0.01 # 10 mH (largest available L)

# Calculate ideal R load ⑦
R_s = mag(Zth+ZL(L_s, freq))
print ("R ideal = %3.3g ohm" % R_s)

R_s = 680 # 680 ohm (nearest value to 739 ohm ideal)

Zload = ZR(R_s)+ZL(L_s, freq)
print ("Z load = %s ohms" % showR(Zload))

```

```
# Compute load parameters (9)
IL = Vth / (Zth + Zload)
print("I load = %s A = (%s A) " % (showR(IL), showP(IL)))

VL = IL * Zload
print("V load = %s V = (%s V) " % (showR(VL), showP(VL)))

SL = VL * Zstar(IL)
print("S load = %s VA = (%s VA) " % (showR(SL), showP(SL)))

# Compute fraction of source power delivered to load
Pload = P(SL)
print("P load = %3.3g% of potential load power " % (100 * (Pload / Pmax)))
```



```
#####
# USERID:.....wbahn
# PROGRAMMER:.....Bahn, William L.
# COURSE:.....EENG-382
# TERM:.....SP14
# PROJECT:.....N/A
# FILENAME:.....z.py
# VERSION:.....1.1
# PYTHON VERSION:..3.3.3
#####

# This file contains simple functions that are useful for
# "scratchpad" Phasor circuit analysis computations.

import cmath

pi = cmath.pi

# Convert R, L, C into complex impedances
def ZR(R): return complex(R, 0)
def ZC(C, fHz): return complex(0, -1/(2*pi*fHz*C))
def ZL(L, fHz): return complex(0, 2*pi*fHz*L)
def ZZ(R, X): return complex(R, X)

# Convert reactance into L or C
def L(X, fHz): return X/(2*pi*fHz)
def C(X, fHz): return -1/(2*pi*fHz*X)

# Combine impedances in series and parallel
def s(Z1, Z2): return Z1 + Z2
def p(Z1, Z2): return (Z1*Z2)/(Z1+Z2)

# Complex conjugate
def Zstar(Z): return complex(Re(Z), -Im(Z))

# Get real/imaginary components (plus aliases)
def Re(z): return z.real
def Im(z): return z.imag
def P(S): return Re(S)
def Q(S): return Im(S)
def R(Z): return Re(Z)
def X(Z): return Im(Z)

# Polar components
def mag(Z): return abs(Z)
def arg(Z): return cmath.phase(Z)
def d2r(deg): return deg*(pi/180)
def r2d(rad): return rad*(180/pi)

# Generate strings for printing
def showR(Z): return ("%4.4g%+4.4gj" % (Re(Z), Im(Z)))
def showP(Z): return ("%4.4g @ %4.4g deg" % (mag(Z), r2d(arg(Z))))
def show(Z): return ("%s = %s" % (showR(Z), showP(Z)))
```