

PROBLEM #1

Consider a Y-connected generator set in which each leg has an open circuit output voltage of 240V and a source impedance of  $(0.1+j0.8) \Omega$ . The transmission lines connecting the generator set to the loads each have an impedance of  $(0.4+j3.2) \Omega$ . The load consists of three Y-connected circuits. The loads are  $Z_A = (59.5+j76) \Omega$ ,  $Z_B = (39.5+j26) \Omega$ , and  $Z_C = (19.5+j11) \Omega$ .

Use the neutral point of the generator set as the voltage reference.

- a) What are the magnitudes of the voltages across and currents in the three loads?
- b) What is the magnitude of the voltage at the neutral point of the load?


A ground rod is now placed at the neutral points of both the generator set and the load and the effective impedance through the ground between the two rods is  $10 \Omega$ .

- c) What are the magnitudes of the voltages across and currents in the three loads?
- d) What is the magnitude of the voltage at the neutral point of the load?
- e) What is the magnitude of the ground current?

In addition to the ground rods, a fourth wire (the same as the others) is added to the transmission line to serve as a neutral wire.

- f) What are the magnitudes of the voltages across and currents in the three loads?
- g) What is the magnitude of the voltage at the neutral point of the load?
- h) What is the magnitude of the ground current?
- i) What is the magnitude of the current in the neutral conductor?

GENERAL CIRCUIT

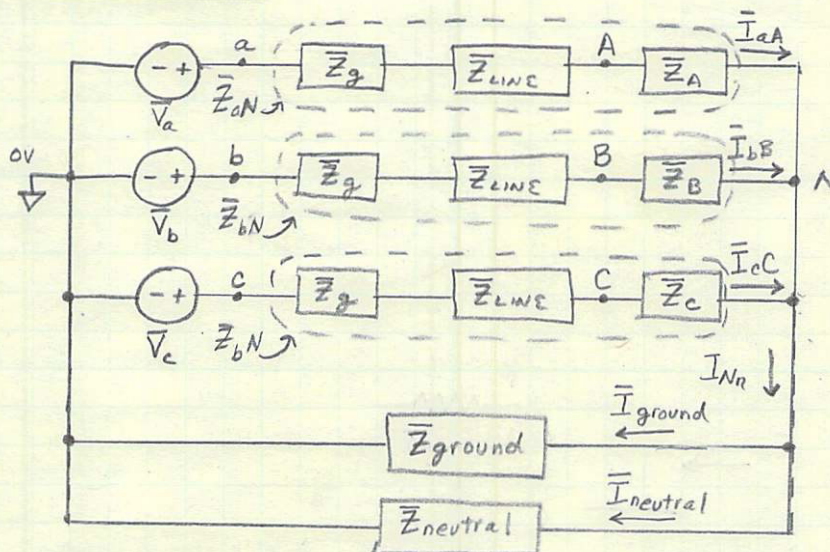

PART	$\bar{Z}_{ground}$	$\bar{Z}_{neutral}$
(a)→(b)	$\infty$	$\infty$
(b)→(e)	$10\Omega$	$\infty$
(f)→(i)	$10\Omega$	$\bar{Z}_{LINE}$

PROBLEM #1 (CONT'D)GENERAL SOLUTION

NODAL ANALYSIS AT NODE N

$$\underbrace{\frac{\bar{V}_a}{\bar{Z}_{aN}} + \frac{\bar{V}_b}{\bar{Z}_{bN}} + \frac{\bar{V}_c}{\bar{Z}_{cN}}}_{\bar{I}_0} = V_N \left( \underbrace{\frac{1}{\bar{Z}_{aN}} + \frac{1}{\bar{Z}_{bN}} + \frac{1}{\bar{Z}_{cN}}}_{\frac{1}{\bar{Z}_{abc}}} + \underbrace{\frac{1}{\bar{Z}_{GROUND}} + \frac{1}{\bar{Z}_{neutral}}}_{\frac{1}{\bar{Z}_N}} \right)$$

$$V_N = \bar{I}_0 \frac{1}{\frac{1}{\bar{Z}_{abc}} + \frac{1}{\bar{Z}_N}}$$

NEUTRAL POINT

$$\text{VOLTAGE IN LOAD: } \bar{V}_N = \bar{I}_0 (\bar{Z}_{abc} \parallel \bar{Z}_N); \quad \bar{Z}_N = \bar{Z}_{GROUND} \parallel \bar{Z}_{neutral}$$

$$\text{LOAD CURRENT: } \bar{I}_{kK} = \frac{\bar{V}_k - \bar{V}_N}{\bar{Z}_{kN}}$$

FOR  $k = \{a, b, c\}$   
(K IS UPPERCASE k)

$$\text{LOAD VOLTAGE: } \bar{V}_{KN} = \bar{I}_{kK} \cdot \bar{Z}_K$$

$$\text{GROUND CURRENT: } \bar{I}_{ground} = \frac{\bar{V}_N}{\bar{Z}_{ground}}$$

$$\text{NEUTRAL CURRENT: } \bar{I}_{neutral} = \frac{\bar{V}_N}{\bar{Z}_{neutral}}$$

COMMON INTERMEDIATE RESULTS

	abc	acb
$\bar{V}_a$	$240V \angle 0^\circ$	$240V \angle 0^\circ$
$\bar{V}_b$	$240V \angle -120^\circ$	$240V \angle +120^\circ$
$\bar{V}_c$	$240V \angle +120^\circ$	$240V \angle -120^\circ$

$$\bar{Z}_g + \bar{Z}_{LINE} = (0.1 + j0.8)\Omega + (0.4 + j3.2)\Omega = (0.5 + j4.0)\Omega$$

$$\bar{Z}_{aN} = (\bar{Z}_g + \bar{Z}_{LINE}) + \bar{Z}_A = (0.5 + j4.0)\Omega + (59.5 + j76)\Omega = (60 + j80)\Omega$$

$$\bar{Z}_{bN} = (\bar{Z}_g + \bar{Z}_{LINE}) + \bar{Z}_B = (0.5 + j4.0)\Omega + (39.5 + j26)\Omega = (40 + j30)\Omega$$

$$\bar{Z}_{cN} = (\bar{Z}_g + \bar{Z}_{LINE}) + \bar{Z}_C = (0.5 + j4.0)\Omega + (19.5 + j11)\Omega = (20 + j15)\Omega$$

$$\bar{Z}_{abc} = (\bar{Z}_{aN} \parallel \bar{Z}_{bN} \parallel \bar{Z}_{cN}) = (11.13 + j9.068)\Omega = 14.36\Omega \angle 39.17^\circ$$

$$\bar{I}_0 = \left( \frac{\bar{V}_a}{\bar{Z}_{aN}} + \frac{\bar{V}_b}{\bar{Z}_{bN}} + \frac{\bar{V}_c}{\bar{Z}_{cN}} \right) = \underbrace{6.010A \angle 107.7^\circ}_{abc} \text{ or } \underbrace{6.877A \angle -172.3^\circ}_{acb}$$

PROBLEM #1 (CONT'D)

A PYTHON SCRIPT WAS WRITTEN TO IMPLEMENT THE GENERAL SOLUTION AND THEN RUN FOR THE THREE CIRCUITS FOR BOTH PHASE SEQUENCES. THE RESULTS FROM THE SCRIPTS ARE PRESENTED BELOW. THE SCRIPT & RUN RESULTS ARE ATTACHED.

		abc		acb		
<u>PART (a)</u>	LOAD	V	I	V	I	
	A	305V	3.16A	305V	3.16A	} ← (#1a)
	B	245V	5.19A	269V	5.70A	
	C	150V	6.71A	130V	5.82A	
<u>PART (b)</u>	$V_N$	86.3V	—	98.7V	—	← (#1b)
<u>PART (c)</u>	LOAD	V	I	V	I	
	A	254V	2.63A	270V	2.80A	} ← (#1c)
	B	245V	5.18A	226V	4.72A	
	C	181V	8.10A	185V	8.28A	
<u>PART (d)</u>	$V_N$	37.5V	—	42.9V	—	← (#1d)
<u>PART (e)</u>	$I_{GND}$	—	3.75A	—	4.29A	← (#1e)
<u>PART (f)</u>	LOAD	V	I	V	I	
	A	246V	2.55A	238V	2.47A	} ← (#1f)
	B	223V	4.71A	238V	5.02A	
	C	206V	9.22A	200V	8.92A	
<u>PART (g)</u>	$V_N$	14.99V	—	17.15V	—	← (#1g)
<u>PART (h)</u>	$I_{GND}$	—	1.499A	—	1.715A	← (#1h)
<u>PART (i)</u>	$I_{NEUTRAL}$	—	4.65A	—	5.32A	← (#1i)

FOR REFERENCE

		abc		acb	
SHORT	LOAD	V	I	V	I
BETWEEN	A	232V	2.40A	232V	2.40A
GEN & LOAD	B	227V	4.80A	227V	4.80A
NEUTRALS	C	215V	9.60A	215V	9.60A
	$V_N$	0V	—	0V	—
	$I_{neu}$	—	6.01A	—	6.88A

ROTATION: abc GROUND: open NEUTRAL: open

VloadA = 304.8 @ -9.777 deg IaA = 3.158 @ -61.72 deg  
 VloadB = 245.4 @ -104.1 deg IbB = 5.189 @ -137.5 deg  
 VloadC = 150.1 @ 99.11 deg IcC = 6.705 @ 69.68 deg  
 VloadN = 86.28 @ 146.9 deg IN = 1.22e-10 @ 101.9 deg  
 Ignd = 6.101e-11 @ 101.9 deg Ineu = 6.101e-11 @ 101.9 deg

ROTATION: abc GROUND: rod NEUTRAL: open

VloadA = 253.5 @ -8.019 deg IaA = 2.626 @ -59.96 deg  
 VloadB = 244.8 @ -116.1 deg IbB = 5.177 @ -149.4 deg  
 VloadC = 181.4 @ 111.9 deg IcC = 8.103 @ 82.46 deg  
 VloadN = 37.52 @ 123.6 deg IN = 3.752 @ 123.6 deg  
 Ignd = 3.752 @ 123.6 deg Ineu = 2.653e-11 @ 78.63 deg

ROTATION: abc GROUND: rod NEUTRAL: line

VloadA = 245.9 @ -1.831 deg IaA = 2.547 @ -53.77 deg  
 VloadB = 222.8 @ -120.1 deg IbB = 4.711 @ -153.4 deg  
 VloadC = 206.4 @ 109.7 deg IcC = 9.218 @ 80.32 deg  
 VloadN = 14.99 @ 169 deg IN = 5.058 @ 103.2 deg  
 Ignd = 1.499 @ 169 deg Ineu = 4.648 @ 86.12 deg

ROTATION: acb GROUND: open NEUTRAL: open

VloadA = 304.8 @ 12.01 deg IaA = 3.158 @ -39.93 deg  
 VloadB = 269.4 @ 97.12 deg IbB = 5.697 @ 63.76 deg  
 VloadC = 130.4 @ -118.6 deg IcC = 5.823 @ -148 deg  
 VloadN = 98.72 @ -133.1 deg IN = 1.396e-10 @ -178.1 deg  
 Ignd = 6.981e-11 @ -178.1 deg Ineu = 6.981e-11 @ -178.1 deg

ROTATION: acb GROUND: rod NEUTRAL: open

VloadA = 270.1 @ 2.345 deg IaA = 2.799 @ -49.6 deg  
 VloadB = 226.1 @ 106.2 deg IbB = 4.782 @ 72.85 deg  
 VloadC = 185.4 @ -120.4 deg IcC = 8.279 @ -149.8 deg  
 VloadN = 42.94 @ -156.3 deg IN = 4.294 @ -156.3 deg  
 Ignd = 4.294 @ -156.3 deg Ineu = 3.036e-11 @ 158.7 deg

ROTATION: acb GROUND: rod NEUTRAL: line

VloadA = 238.1 @ 2.536 deg IaA = 2.467 @ -49.41 deg  
 VloadB = 237.5 @ 113.4 deg IbB = 5.023 @ 80.09 deg  
 VloadC = 199.8 @ -128.1 deg IcC = 8.923 @ -157.6 deg  
 VloadN = 17.15 @ -111 deg IN = 5.788 @ -176.7 deg  
 Ignd = 1.715 @ -111 deg Ineu = 5.319 @ 166.2 deg

ROTATION: abc GROUND: open NEUTRAL: short

VloadA = 231.6 @ -1.187 deg IaA = 2.4 @ -53.13 deg  
 VloadB = 227 @ -123.5 deg IbB = 4.8 @ -156.9 deg  
 VloadC = 214.9 @ 112.6 deg IcC = 9.6 @ 83.13 deg  
 VloadN = 8.499e-12 @ 152.7 deg IN = 6.01 @ 107.7 deg  
 Ignd = 6.01e-24 @ 107.7 deg Ineu = 6.01 @ 107.7 deg

ROTATION: acb GROUND: open NEUTRAL: short

VloadA = 231.6 @ -1.187 deg IaA = 2.4 @ -53.13 deg  
 VloadB = 227 @ 116.5 deg IbB = 4.8 @ 83.13 deg  
 VloadC = 214.9 @ -127.4 deg IcC = 9.6 @ -156.9 deg  
 VloadN = 9.725e-12 @ -127.3 deg IN = 6.877 @ -172.3 deg  
 Ignd = 6.877e-24 @ -172.3 deg Ineu = 6.877 @ -172.3 deg

```
#####  
# USERID:..... wbahn  
# PROGRAMMER:..... Bahn, William L.  
# COURSE:..... EENG-382  
# TERM:..... SP14  
# PROJECT:..... N/A  
# FILENAME:..... HW03.py  
# PYTHON VERSION:. 3.3.3  
#####
```

```
from z import *
```

```
def hw03(seq, rod, neutral):
```

```
    # Generator Sequence
```

```
    Va = PhP(240, 0)
```

```
    if (seq == "abc"):
```

```
        Vb = PhP(240, -120)
```

```
        Vc = PhP(240, +120)
```

```
    else:
```

```
        Vb = PhP(240, +120)
```

```
        Vc = PhP(240, -120)
```

```
    # Impedances
```

```
    Zs = PhR(0.1, 0.8)
```

```
    ZloadA = PhR(59.5, 76)
```

```
    ZloadB = PhR(39.5, 26)
```

```
    ZloadC = PhR(19.5, 11)
```

```
    Zline = PhR(0.4, 3.2)
```

```
    Zground = PhR(10, 0)
```

```
    Zopen = PhR(1e12, 1e12)
```

```
    # Set ground rod impedance
```

```
    Zgnd = Zopen
```

```
    if (rod == "rod"):
```

```
        Zgnd = Zground
```

```
    # Set neutral bond impedance
```

```
    Zneu = Zopen
```

```
    if (neutral == "line"):
```

```
        Zneu = Zline
```

```
    if (neutral == "short"):
```

```
        Zneu = PhR(1e-12, 1e-12)
```

```
    # Total Phase Impedances
```

```
    ZA = Zs + Zline + ZloadA
```

```
    ZB = Zs + Zline + ZloadB
```

```
    ZC = Zs + Zline + ZloadC
```

```
# Intermediate results
Io = Va/ZA + Vb/ZB + Vc/ZC
ZABC = 1/(1/ZA + 1/ZB + 1/ZC)

ZN = p(Zgnd, Zneu)
ZABCN = 1/(1/ZABC + 1/ZN)
VN = Io*ZABCN
IN = VN/ZN
Ignd = VN/Zgnd
Ineu = VN/Zneu
IaA = (Va-VN)/ZA
IbB = (Vb-VN)/ZB
IcC = (Vc-VN)/ZC
VAN = IaA*ZloadA
VBN = IbB*ZloadB
VCN = IcC*ZloadC

print()
print("ROTATION: %s GROUND: %s NEUTRAL: %s" % (seq, rod, neutral))
print("VloadA = %s IaA = %s" % (showP(VAN), showP(IaA)))
print("VloadB = %s IbB = %s" % (showP(VBN), showP(IbB)))
print("VloadC = %s IcC = %s" % (showP(VCN), showP(IcC)))
print("VloadN = %s IN = %s" % (showP(VN), showP(IN)))
print("Ignd = %s Ineu = %s" % (showP(Ignd), showP(Ineu)))

hw03("abc", "open", "open")
hw03("abc", "rod", "open")
hw03("abc", "rod", "line")

hw03("acb", "open", "open")
hw03("acb", "rod", "open")
hw03("acb", "rod", "line")

hw03("abc", "open", "short")
hw03("acb", "open", "short")
```