


PROBLEM 13.11

13.11 The switch in the circuit in Fig. P13.11 has been closed for a long time before opening at $t = 0$.


PSPICE
MULTISIM

- a) Construct the s -domain equivalent circuit for $t > 0$.
- b) Find V_o .
- c) Find v_o for $t \geq 0$.

Figure P13.11

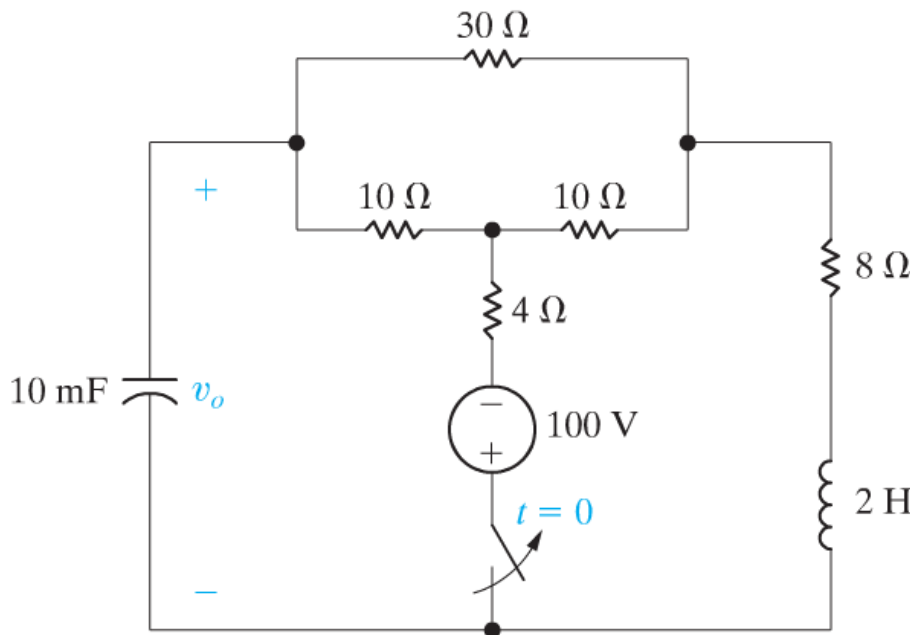

CIRCUIT TO FIND INITIAL CONDITIONS

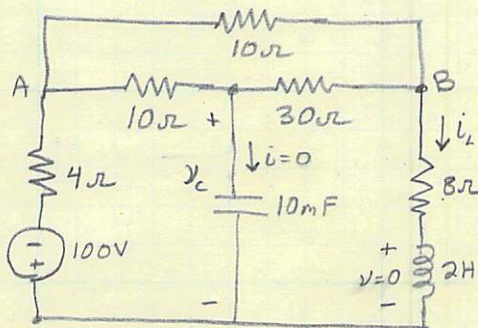

$$i_L = \frac{-100V}{8\Omega + 4\Omega + (10\Omega \parallel (10\Omega + 30\Omega))}$$

$$i_L = \frac{-100V}{12\Omega + \frac{400\Omega^2}{50\Omega}} = \frac{-100V}{20\Omega} = -5A$$


$$V_A = -100V - (-5A)(4\Omega) = -80V$$

$$V_B = (-5A)(8\Omega) = -40V$$

$$V_c = V_B + (V_A - V_B) \cdot \frac{30\Omega}{10\Omega + 30\Omega} = -40V + -40V \cdot \frac{3}{4}$$

$$V_c = -40V - 30V = -70V$$

PROBLEM 13.11 (CONT'D)

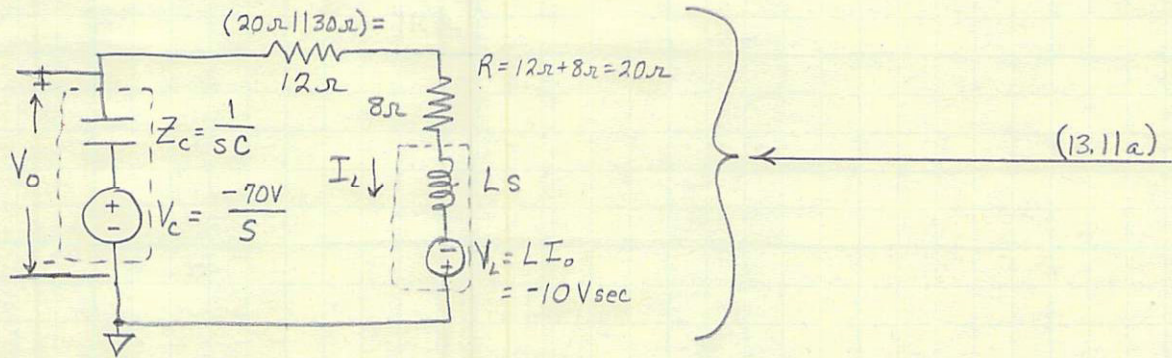

$$\text{NODAL: } V_o \left(\frac{1}{Z_c} + \frac{1}{R + Ls} \right) - V_c \left(\frac{1}{Z_c} \right) - (-V_L) \left(\frac{1}{R + Ls} \right) = 0$$

$$V_o \left(Cs + \frac{1}{Ls + R} \right) = \frac{10Vsec}{(R + Ls)} - \frac{70V}{s} \cdot sC$$

$$V_o \left(\frac{LCs^2 + RCs + 1}{Ls + R} \right) = \frac{10Vsec - RC(70V) - LCs(70V)}{(R + Ls)}$$

$$V_o = \frac{-[LC \cdot 70V] \cdot s + (70V \cdot RC - 10V \cdot sec)}{(LCs^2 + RCs + 1)}$$

$$V_o = \frac{-70V \cdot LC \left(s + \left(\frac{R}{L} - \frac{10V \cdot sec}{70V \cdot LC} \right) \right)}{LC \left(s^2 + \left(\frac{R}{L} \right) s + \left(\frac{1}{LC} \right) \right)}$$

$$\frac{R}{L} = \frac{20\Omega}{2H} = 10r/sec; \quad \frac{1}{LC} = \frac{1}{2H \cdot 10mF} = 50r^2/sec^2$$

$$\frac{R}{L} - \frac{50r}{7} / sec = \left(\frac{70}{7} - \frac{50}{7} \right) r/sec = \frac{20}{7} r/sec$$

$$V_o = -70V \frac{s + \left(\frac{20}{7} r/sec \right)}{s^2 + (10r/sec)s + (50r^2/sec^2)} \quad \leftarrow (13.11b)$$

$$s_0, s_1 = -\frac{10r/sec}{2} \pm \sqrt{25r^2/sec^2 - 50r^2/sec^2} = -5r/sec \pm j5r/sec = -\alpha \pm j\beta$$

$$V_o = -70V \left[\frac{K_1}{s + [5r/sec(1+j)]} + \frac{K_1^*}{s + [5r/sec(1-j)]} \right]$$

$$K_1 = \left. \frac{(s + \frac{20}{7} r/sec)}{s + [5r/sec(1-j)]} \right|_{s = -(5r/sec)(1+j)} = \frac{-5r/sec + \frac{20}{7} r/sec - j5r/sec}{-j10r/s}$$

$$K_1 = \frac{1}{2} \left(1 - j \frac{3}{7} \right) = 0.5440 \angle -156.80^\circ$$

$$V_o = -70V \left[\frac{K_1}{s + (-s_1)} + \frac{K_1^*}{s + (-s_1^*)} \right] = -70V |K| \left[\frac{1 \angle \theta_K}{s + (-s_1)} + \frac{1 \angle \theta_K}{s + (-s_1^*)} \right]$$

$$v(t) = -70V \cdot |K| \left[e^{j\theta_K} e^{-\alpha t} e^{-j\omega t} + e^{-j\theta_K} e^{-\alpha t} e^{j\omega t} \right] = -70V \cdot |K| e^{-\alpha t} \cdot 2 \cos(\omega t - \theta_K)$$

$$v(t) = -70V \cdot (0.5440) \cdot (2) e^{-5r/s t} \cos(5r/s t + 156.80^\circ)$$

$$v(t) = +76.2V e^{-\left(\frac{t}{200ms}\right)} \cos((5r/s)t - 156.8^\circ) \quad \leftarrow (13.11c)$$

$$\text{CHECK: } v(t=0) \stackrel{?}{=} -70V = 76.2V \cos(-156.80^\circ) = 76.2V \cdot (-0.9191) = -70.0V \checkmark$$


PROBLEM # 13.36

13.36 The magnetically coupled coils in the circuit seen in Fig. P13.36 carry initial currents of 15 and 10 A, as shown.

PSPICE
MULTISIM


- Find the initial energy stored in the circuit.
- Find I_1 and I_2 .
- Find i_1 and i_2 .
- Find the total energy dissipated in the 120 and 270 Ω resistors.
- Repeat (a)–(d), with the dot on the 18 H inductor at the lower terminal.

Figure P13.36

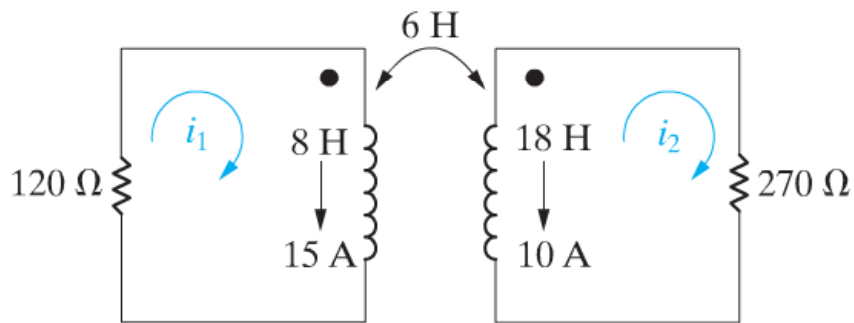

IF FOR NO OTHER REASON, BECAUSE WE HAVE TO REPEAT EVERYTHING WITH THE DOTS MOVED, WE WILL WORK THE PROBLEM SYMBOLICALLY.

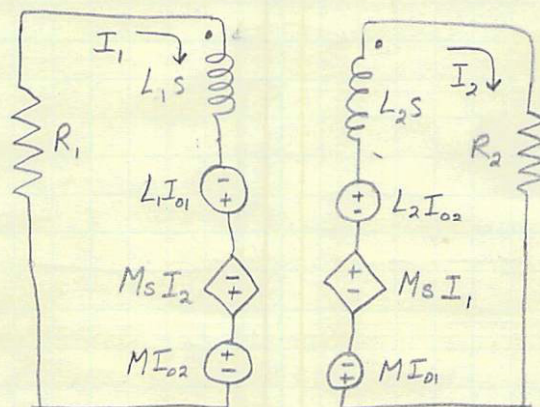ALSO, IF $M=0$ WE KNOW THE ANSWERS BY INSPECTION SINCE EACH SIDE IS INDEPENDENT AND A SIMPLE LR FIRST-ORDER CIRCUIT. THIS PROVIDES AN OBVIOUS SANITY CHECK.



PROBLEM #13.36 (CONT'D)

$$U = \frac{1}{2} L_1 \dot{I}_1^2 + \frac{1}{2} L_2 \dot{I}_2^2 + M \dot{I}_1 \dot{I}_2 \quad (\text{EQN 6.66})$$

NOTE: \dot{I}_1, \dot{I}_2 ARE THE CURRENTS ENTERING THE POLARITY MARKED TERMINAL.

$$U_{\text{TOT}} = \frac{1}{2} (8H)(15A)^2 + \frac{1}{2} (18H)(-10A)^2 - (6H)(15A)(-10A)$$

$$\therefore U_{\text{TOT}} = 2700 \text{ J}$$

$$\begin{aligned} I_1 (R_1 + L_1 s) - I_2 (M s) &= L_1 I_{o1} - M I_{o2} \\ -I_1 (M s) + I_2 (R_2 + L_2 s) &= L_2 I_{o2} - M I_{o1} \end{aligned}$$

NOTING THE SYMMETRY OF THE ABOVE EQUATIONS, WE CAN SOLVE FOR I_1 , AND OBTAIN THE SOLUTION FOR I_2 BY SWAPPING '1' & '2' SUBSCRIPTS.

$$I_1 [(R_1 + L_1 s)(R_2 + L_2 s) - (M s)^2] = (L_1 I_{o1} - M I_{o2})(R_2 + L_2 s) + (L_2 I_{o2} - M I_{o1})(M s)$$

$$I_1 = \frac{s(L_1 I_{o1} L_2 - M L_2 I_{o2} + M L_1 I_{o2} - M^2 I_{o1}) + R_2 (L_1 I_{o1} - M I_{o2})}{(L_1 L_2 - M^2) s^2 + (R_1 L_2 + R_2 L_1) s + R_1 R_2}$$

$$I_1 = I_{o1} \frac{\left(s + \frac{R_2 (L_1 I_{o1} - M I_{o2})}{I_{o1} (L_1 L_2 - M^2)} \right)}{s^2 + \frac{(R_1 L_2 + R_2 L_1)}{(L_1 L_2 - M^2)} s + \frac{R_1 R_2}{(L_1 L_2 - M^2)}}$$

$$s_0, s_1 = \frac{1}{2} \left[\frac{-(R_1 L_2 + R_2 L_1)}{(L_1 L_2 - M^2)} \pm \sqrt{\frac{(R_1 L_2)^2 + R_1 R_2 L_1 L_2 + (R_2 L_1)^2}{(L_1 L_2 - M^2)^2} - \frac{4 R_1 R_2 (L_1 L_2 - M^2)}{(L_1 L_2 - M^2)^2}} \right]$$

$$s_0, s_1 = \frac{-(R_1 L_2 + R_2 L_1) \pm \sqrt{(R_1 L_2 - R_2 L_1)^2 + 4 R_1 R_2 M^2}}{2 (L_1 L_2 - M^2)}$$

CHECK: IF $M=0$: $s_0, s_1 = -\frac{R_1}{L_1}, -\frac{R_2}{L_2}$; $I_1 = I_{o1} \frac{(s + \frac{R_2}{L_2})}{(s + R_1/L_1)(s + R_2/L_2)}$ ✓

$$I_1 = I_{o1} \frac{(s + z_1)}{(s - s_0)(s - s_1)}$$

FOR I_1 : $z_1 = \frac{(270\Omega)[(8H)(15A) - (6H)(-10A)]}{(15A)[(8H)(18H) - (6H)^2]} = \frac{(270\Omega)(180HA)}{(15A)(108H^2)} = 30 \text{ } \Omega/\text{s}$

$$(R_1 L_2 - R_2 L_1) = (120\Omega)(18H) - (270\Omega)(8H) = 0$$

$$(R_1 L_2 + R_2 L_1) = (120\Omega)(18H) + (270\Omega)(8H) = 4320\Omega H$$

$$\sqrt{4 R_1 R_2 M^2} = 2(6H)\sqrt{(120\Omega)(270\Omega)} = 2160\Omega H$$

$$L_1 L_2 - M^2 = (8H)(18H) - (6H)^2 = 108H^2$$

FOR I_1 : $s_0, s_1 = \frac{-4320\Omega H \pm 2160\Omega H}{2 \cdot 108H^2} = (-20 \pm 10) \frac{\Omega}{H} = -30 \text{ } \Omega/\text{s}, -10 \text{ } \Omega/\text{s}$

FOR I_2 : $z_1 = \frac{(120\Omega)[(18H)(-10A) - (6H)(15A)]}{(-10A)(108H^2)} = 30 \text{ } \Omega/\text{s}$

$s_0, s_1 = \text{SAME AS FOR } I_1$

PROBLEM # 13.36 (CONT'D)

$$I_1 = I_{01} \frac{(s+z_1)}{(s-s_0)(s-s_1)} = 15A \frac{(s+30r/s)}{(s+30r/s)(s+10r/s)}$$

$$I_2 = I_{02} \frac{s+z_1}{(s-s_1)(s-s_2)} = -10A \frac{(s+30r/s)}{(s+30r/s)(s+10r/s)}$$

$$\left. \begin{aligned} I_1 &= \frac{15A}{(s+10r/s)} \\ I_2 &= \frac{-10A}{(s+10r/s)} \end{aligned} \right\} \leftarrow \text{(#13.36b)}$$

$$\left. \begin{aligned} i_1(t) &= 15A e^{-(10r/s)t} u(t) \\ i_2(t) &= -10A e^{-(10r/s)t} u(t) \end{aligned} \right\} \leftarrow \text{(#13.36c)}$$

FOR AN EXPONENTIAL CURRENT THROUGH A RESISTOR:

$$U = \int_{-\infty}^{\infty} i^2(t) \cdot R \cdot dt = R \int_{-\infty}^{\infty} (I_0 e^{-\alpha t} u(t))^2 dt$$

$$= I_0^2 R \int_0^{\infty} e^{-2\alpha t} dt = I_0^2 R \left(\frac{-1}{2\alpha} \right) e^{-2\alpha t} \Big|_0^{\infty}$$

$$U = \frac{I_0^2 R}{2\alpha}$$

$$\left. \begin{aligned} U_{R1} &= \frac{(15A)^2 (120\Omega)}{2 \cdot 10r/s} = 1350J \\ U_{R2} &= \frac{(-10A)^2 (270\Omega)}{2 \cdot 10r/s} = 1350J \end{aligned} \right\} \leftarrow \text{(#13.36d)}$$

$$U_{TOT} = U_{R1} + U_{R2} = 2700J \checkmark$$

SWITCHING THE DOT LOCATION ON ONE INDUCTOR EFFECTUALLY MAKE $M \Rightarrow -M$.
TRACKING THIS CHANGE THROUGH THE PRIOR WORK YIELDS:

$$U_{TOT} = \frac{1}{2} (8H)(15A)^2 + \frac{1}{2} (18H)(-10A)^2 - (-6H)(15A)(-10A) = 900J \leftarrow \text{(a) (#13.36e)}$$

$$I_1: Z_1 = \frac{(270\Omega)[(8H)(15A) - (-6H)(-10A)]}{(15A)(108H^2)} = 10r/s$$

$$I_2: Z_1 = \frac{(120\Omega)[(18H)(-10A) - (-6H)(15A)]}{(-10A)(108H^2)} = 10r/s$$

THE POLE LOCATIONS ARE UNCHANGED.

$$I_1 = \frac{15A}{(s+30r/s)} ; I_2 = \frac{-10A}{(s+30r/s)} \leftarrow \text{(b)}$$

$$i_1(t) = 15A e^{-(30r/s)t} u(t) ; i_2(t) = -10A e^{-(30r/s)t} u(t) \leftarrow \text{(c)}$$

$$U_1 = \frac{(15A)^2 (120\Omega)}{2(30r/s)} = 450J ; U_2 = \frac{(-10A)^2 (270\Omega)}{2(30r/s)} = 450J \leftarrow \text{(d)}$$

$$U_T = U_1 + U_2 = 900J \checkmark$$