

EENG 281 Homework #5 Solutions  
Fall 2013

P 5.6 [a]  $i_2 = \frac{150 \times 10^{-3}}{2000} = 75 \mu\text{A}$

$$v_1 = -40 \times 10^3 i_2 = -3 \text{ V}$$

[b]  $\frac{v_1}{20,000} + \frac{v_1}{40,000} + \frac{v_1 - v_o}{50,000} = 0$

$$\therefore v_o = 4.75v_1 = -14.25 \text{ V}$$

[c]  $i_2 = 75 \mu\text{A}$ , (from part [a])

[d]  $i_o = \frac{-v_o}{25,000} + \frac{v_1 - v_o}{50,000} = 795 \mu \text{ A}$

P 5.26 Use voltage division to find  $v_p$ :

$$v_p = \frac{2000}{2000 + 8000}(5) = 1 \text{ V}$$

Write a KCL equation at  $v_n$  and solve it for  $v_o$ :

$$\frac{v_n - v_a}{5000} + \frac{v_n - v_o}{R_f} = 0 \quad \text{so} \quad \left(\frac{R_f}{5000} + 1\right)v_n - \frac{R_f}{5000}v_o = v_a$$

Since the op amp is ideal,  $v_n = v_p = 1\text{V}$ , so

$$v_o = \left(\frac{R_f}{5000} + 1\right)v_n - \frac{R_f}{5000}v_a$$

To satisfy the equation,

$$\left(\frac{R_f}{5000} + 1\right) = 5 \quad \text{and} \quad \frac{R_f}{5000} = 4$$

Thus,  $R_f = 20 \text{ k}\Omega$ .


P 5.36 It follows directly from the circuit that  $v_o = -(120/7.5)v_g = -16v_g$   
 From the plot of  $v_g$  we have  $v_g = 0, \quad t < 0$

$$\begin{aligned} v_g &= t & 0 \leq t \leq 0.5 \\ v_g &= 1 - t & 0.5 \leq t \leq 1.5 \\ v_g &= t - 2 & 1.5 \leq t \leq 2.5 \\ v_g &= 3 - t & 2.5 \leq t \leq 3.5 \\ v_g &= t - 4 & 3.5 \leq t \leq 4.5, \text{ etc.} \end{aligned}$$

Therefore

$$\begin{aligned} v_o &= -16t & 0 \leq t \leq 0.5 \\ v_o &= 16t - 16 & 0.5 \leq t \leq 1.5 \\ v_o &= 32 - 16t & 1.5 \leq t \leq 2.5 \\ v_o &= 16t - 48 & 2.5 \leq t \leq 3.5 \\ v_o &= 64 - 16t & 3.5 \leq t \leq 4.5, \text{ etc.} \end{aligned}$$

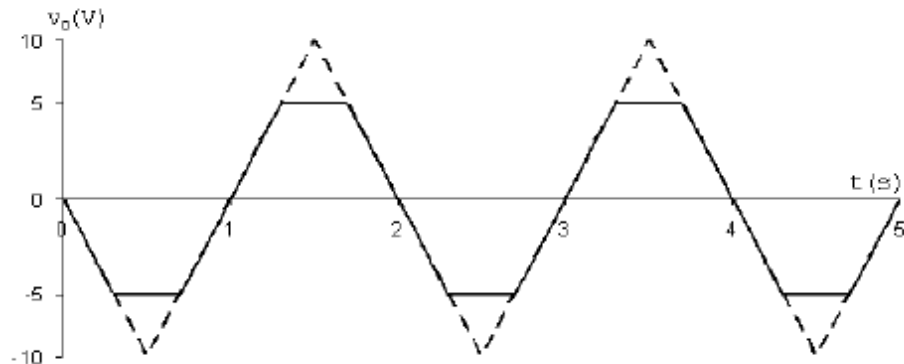These expressions for  $v_o$  are valid as long as the op amp is not saturated.  
 Since the peak values of  $v_o$  are  $\pm 5$ , the output is clipped at  $\pm 5$ . The plot is shown below.



P 5.39 [a]  $p_{16\text{k}\Omega} = \frac{(320 \times 10^{-3})^2}{(16 \times 10^3)} = 6.4 \mu\text{W}$

[b]  $v_{16\text{k}\Omega} = \left(\frac{16}{64}\right)(320) = 80\text{mV}$

$$p_{16\text{k}\Omega} = \frac{(80 \times 10^{-3})^2}{(16 \times 10^3)} = 0.4 \mu\text{W}$$

[c]  $\frac{p_a}{p_b} = \frac{6.4}{0.4} = 16$

[d] Yes, the operational amplifier serves several useful purposes:

- First, it enables the source to control 16 times as much power delivered to the load resistor. When a small amount of power controls a larger amount of power, we refer to it as *power amplification*.
- Second, it allows the full source voltage to appear across the load resistor, no matter what the source resistance. This is the *voltage follower* function of the operational amplifier.
- Third, it allows the load resistor voltage (and thus its current) to be set without drawing any current from the input voltage source. This is the *current amplification* function of the circuit.