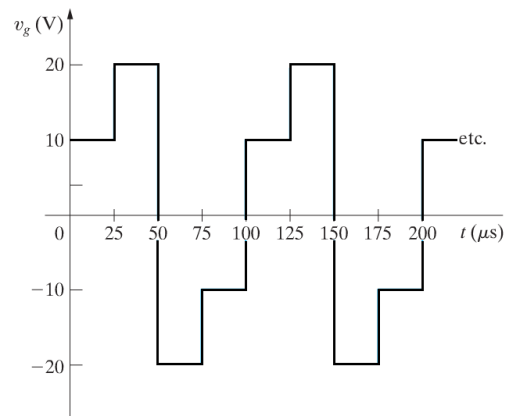


**Problem #1 (12 pts)**

- 10.15** a) Find the rms value of the periodic voltage shown in Fig. P10.15.
- b) If this voltage is applied to the terminals of a  $4\ \Omega$  resistor, what is the average power dissipated in the resistor?

Figure P10.15




**Problem #2 (16 pts)**

A balanced Y-connected load having an impedance of  $(80+j60) \Omega/\phi$  is connected to a  $\Delta$ -connected source in which each generator is producing 10kV (rms).

- a) What is the apparent power produced by the generator set?
- b) What is the real power consumed by the load?
- c) What is the complex power produced by the generator set?
- b) What is the power factor of the load?

**Problem #3 (12 pts)**

- 10.44** a) Determine the load impedance for the circuit shown in Fig. P10.44 that will result in maximum average power being transferred to the load if  $\omega = 5 \text{ krad/s}$ .

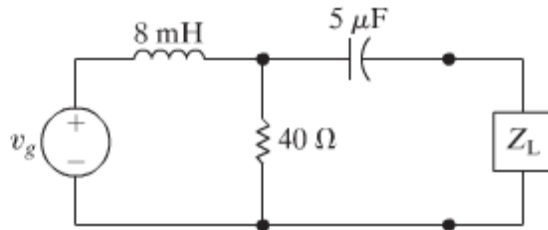**Figure P10.44**

**Problem #4 (10 pts)**

Find the one-sided Laplace transform of the following function beginning with the definition of the one-sided Laplace transform.

$$e^{-at} \sin \omega t$$

(damped sine)

**Problem #5 (10 pts)**

Prove/derive the following operational Laplace transform.

$$tf(t)$$

$$- \frac{dF(s)}{ds}$$

**TABLE OF LAPLACE TRANSFORMS**

An Abbreviated List of Laplace Transform Pairs		
$f(t)$ ( $t > 0^-$ )	Type	$F(s)$
$\delta(t)$	(impulse)	1
$u(t)$	(step)	$\frac{1}{s}$
$t$	(ramp)	$\frac{1}{s^2}$
$e^{-at}$	(exponential)	$\frac{1}{s+a}$
$\sin \omega t$	(sine)	$\frac{\omega}{s^2 + \omega^2}$
$\cos \omega t$	(cosine)	$\frac{s}{s^2 + \omega^2}$
$te^{-at}$	(damped ramp)	$\frac{1}{(s+a)^2}$
$e^{-at} \sin \omega t$	(damped sine)	$\frac{\omega}{(s+a)^2 + \omega^2}$
$e^{-at} \cos \omega t$	(damped cosine)	$\frac{s+a}{(s+a)^2 + \omega^2}$

An Abbreviated List of Operational Transforms	
$f(t)$	$F(s)$
$Kf(t)$	$KF(s)$
$f_1(t) + f_2(t) - f_3(t) + \dots$	$F_1(s) + F_2(s) - F_3(s) + \dots$
$\frac{df(t)}{dt}$	$sF(s) - f(0^-)$
$\frac{d^2 f(t)}{dt^2}$	$s^2 F(s) - sf(0^-) - \frac{df(0^-)}{dt}$
$\frac{d^n f(t)}{dt^n}$	$s^n F(s) - s^{n-1} f(0^-) - s^{n-2} \frac{df(0^-)}{dt} - s^{n-3} \frac{d^2 f(0^-)}{dt^2} - \dots - \frac{d^{n-1} f(0^-)}{dt^{n-1}}$
$\int_0^t f(x) dx$	$\frac{F(s)}{s}$
$f(t-a)u(t-a), a > 0$	$e^{-as} F(s)$
$e^{-at} f(t)$	$F(s+a)$
$f(at), a > 0$	$\frac{1}{a} F\left(\frac{s}{a}\right)$
$tf(t)$	$-\frac{dF(s)}{ds}$
$t^n f(t)$	$(-1)^n \frac{d^n F(s)}{ds^n}$
$\frac{f(t)}{t}$	$\int_s^\infty F(u) du$