

EENG282 HW01 – AUTHOR'S SOLUTIONS

NOTE: I have not yet verified that the author's solutions are, in fact, correct.

Prob. 9.8

$$P\ 9.8 \quad V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^{T/2} V_m^2 \sin^2 \frac{2\pi}{T} t \, dt}$$

$$\int_0^{T/2} V_m^2 \sin^2 \left(\frac{2\pi}{T} t \right) \, dt = \frac{V_m^2}{2} \int_0^{T/2} \left(1 - \cos \frac{4\pi}{T} t \right) \, dt = \frac{V_m^2 T}{4}$$

$$\text{Therefore } V_{\text{rms}} = \sqrt{\frac{1}{T} \frac{V_m^2 T}{4}} = \frac{V_m}{2}$$

Prob. 9.17

$$P\ 9.17 \quad [a] \quad Z_1 = R_1 + j\omega L_1$$

$$Z_2 = \frac{R_2(j\omega L_2)}{R_2 + j\omega L_2} = \frac{\omega^2 L_2^2 R_2 + j\omega L_2 R_2^2}{R_2^2 + \omega^2 L_2^2}$$

$$Z_1 = Z_2 \quad \text{when} \quad R_1 = \frac{\omega^2 L_2^2 R_2}{R_2^2 + \omega^2 L_2^2} \quad \text{and} \quad L_1 = \frac{R_2^2 L_2}{R_2^2 + \omega^2 L_2^2}$$

$$[b] \quad R_1 = \frac{(4000)^2 (1.25)^2 (5000)}{5000^2 + 4000^2 (1.25)^2} = 2500 \, \Omega$$

$$L_1 = \frac{(5000)^2 (1.25)}{5000^2 + 4000^2 (1.25)^2} = 625 \, \text{mH}$$

Prob. 9.20

P 9.20 [a] $Y_2 = \frac{1}{R_2} + j\omega C_2$

$$Y_1 = \frac{1}{R_1 + (1/j\omega C_1)} = \frac{j\omega C_1}{1 + j\omega R_1 C_1} = \frac{\omega^2 R_1 C_1^2 + j\omega C_1}{1 + \omega^2 R_1^2 C_1^2}$$

Therefore $Y_1 = Y_2$ when


$$R_2 = \frac{1 + \omega^2 R_1^2 C_1^2}{\omega^2 R_1 C_1^2} \quad \text{and} \quad C_2 = \frac{C_1}{1 + \omega^2 R_1^2 C_1^2}$$

[b] $R_2 = \frac{1 + (50 \times 10^3)^2 (1000)^2 (40 \times 10^{-9})^2}{(50 \times 10^3)^2 (1000) (40 \times 10^{-9})^2} = 1250 \Omega$

$$C_2 = \frac{40 \times 10^{-9}}{1 + (50 \times 10^3)^2 (1000)^2 (40 \times 10^{-9})^2} = 8 \text{ nF}$$

Prob. 9.35

P 9.35

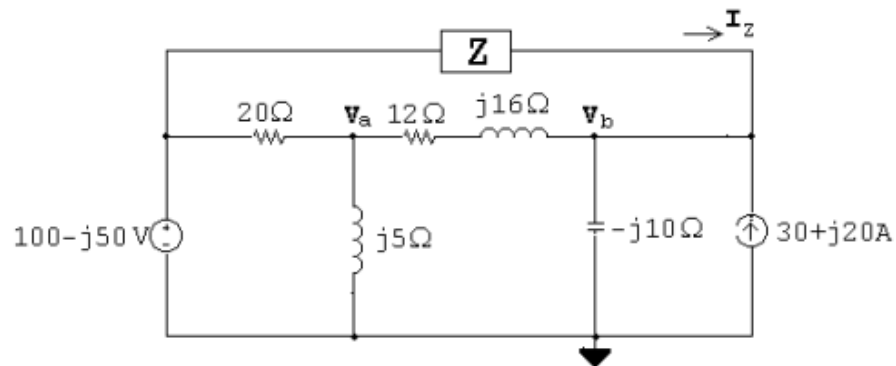

$$\frac{V_a - (100 - j50)}{20} + \frac{V_a}{j5} + \frac{V_a - (140 + j30)}{12 + j16} = 0$$

Solving,

$$V_a = 40 + j30 \text{ V}$$

$$I_Z + (30 + j20) - \frac{140 + j30}{-j10} + \frac{(40 + j30) - (140 + j30)}{12 + j16} = 0$$


Solving,

$$I_Z = -30 - j10 \text{ A}$$

$$Z = \frac{(100 - j50) - (140 + j30)}{-30 - j10} = 2 + j2 \Omega$$

Prob. 9.48

Open circuit voltage:

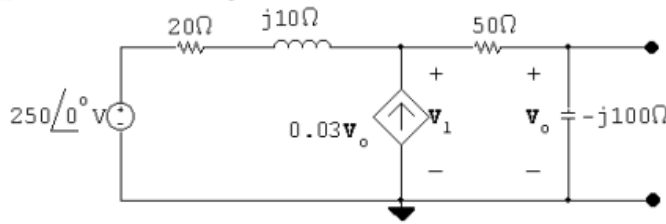


$$\frac{V_1 - 250}{20 + j10} - 0.03V_o + \frac{V_1}{50 - j100} = 0$$

$$\therefore V_o = \frac{-j100}{50 - j100} V_1$$

$$\frac{V_1}{20 + j10} + \frac{j3V_1}{50 - j100} + \frac{V_1}{50 - j100} = \frac{250}{20 + j10}$$

$$V_1 = 500 - j250 \text{ V}; \quad V_o = 300 - j400 \text{ V} = V_{Th}$$


Short circuit current:

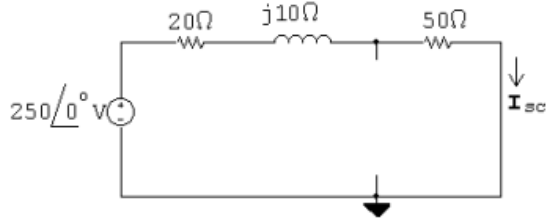

$$I_{sc} = \frac{250/0^\circ}{70 + j10} = 3.5 - j0.5 \text{ A}$$

$$Z_{Th} = \frac{V_{Th}}{I_{sc}} = \frac{300 - j400}{3.5 - j0.5} = 100 - j100 \Omega$$


The Thévenin equivalent circuit:

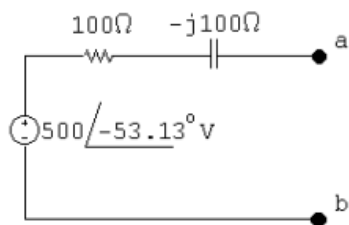

Prob. 9.67

$$P\ 9.67 \quad \frac{1}{j\omega C_1} = -j10\text{ k}\Omega$$
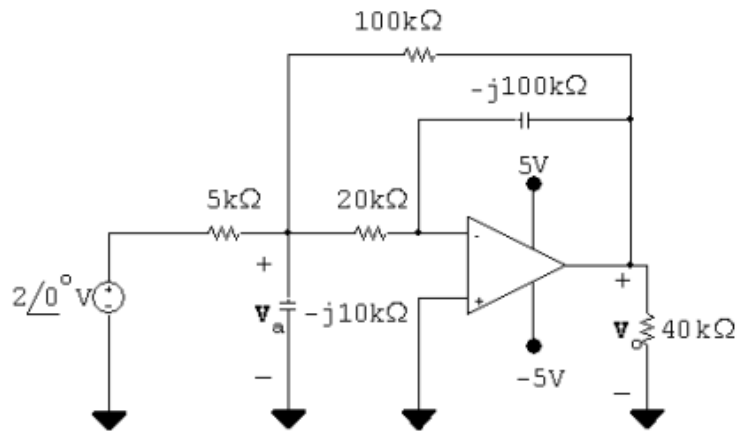
$$\frac{1}{j\omega C_2} = -j100\text{ k}\Omega$$



$$\frac{V_a - 2}{5000} + \frac{V_a}{-j10,000} + \frac{V_a}{20,000} + \frac{V_a - V_o}{100,000} = 0$$

$$20V_a - 40 + j10V_a + 5V_a + V_a - V_o = 0$$

$$\therefore (26 + j10)V_a - V_o = 40$$

$$\frac{0 - V_a}{20,000} + \frac{0 - V_o}{-j100,000} = 0$$

$$j5V_a - V_o = 0$$

Solving,

$$V_o = 1.43 + j7.42 = 7.56/\underline{79.09^\circ} \text{ V}$$

$$v_o(t) = 7.56 \cos(10^6 t + 79.09^\circ) \text{ V}$$

Prob. 9.79

$$P \ 9.79 \quad j\omega L_1 = j50 \ \Omega$$

$$j\omega L_2 = j32 \ \Omega$$

$$\frac{1}{j\omega C} = -j20 \ \Omega$$

$$j\omega M = j(4 \times 10^3)k\sqrt{(12.5)(8)} \times 10^{-3} = j40k \ \Omega$$

$$Z_{22} = 5 + j32 - j20 = 5 + j12 \ \Omega$$

$$Z_{22}^* = 5 - j12 \ \Omega$$

$$Z_r = \left[\frac{40k}{|5 + j12|} \right]^2 (5 - j12) = 47.337k^2 - j113.609k^2$$

$$Z_{ab} = 20 + j50 + 47.337k^2 - j113.609k^2 = (20 + 47.337k^2) + j(50 - 113.609k^2)$$

Z_{ab} is resistive when

$$50 - 113.609k^2 = 0 \quad \text{or} \quad k^2 = 0.44 \quad \text{so} \quad k = 0.66$$

$$\therefore Z_{ab} = 20 + (47.337)(0.44) = 40.83 \ \Omega$$