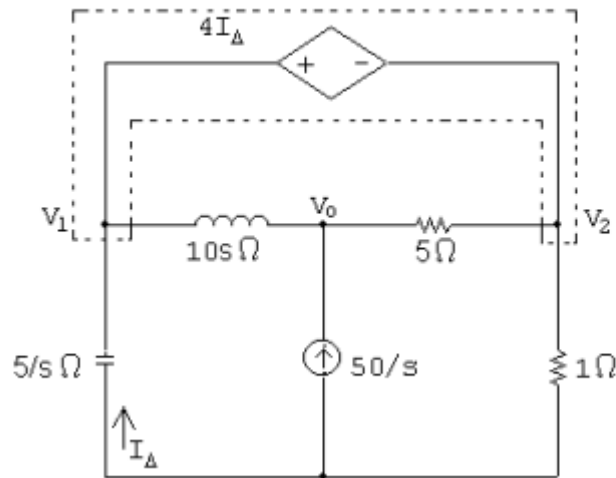


EENG382 QZ02 – AUTHOR'S SOLUTIONS

NOTE: I have not yet verified that the author's solutions are, in fact, correct.

Prob 13.30

P 13.30 [a]



At V_o :

$$\frac{V_o - V_1}{10s} - \frac{50}{s} + \frac{V_o - V_2}{5} = 0$$

$$\therefore V_o(2s + 1) - 2sV_2 - V_1 = 500$$

Supernode:

$$\frac{V_1s}{5} + \frac{V_1 - V_o}{10s} + \frac{V_2}{1} + \frac{V_2 - V_1}{5} = 0$$

$$\therefore -V_o(2s + 1) + 12sV_2 + (2s^2 + 1)V_1 = 0$$

Prob 13.30 (Cont'd)

Constraint:

$$V_1 - V_2 = 4I_\Delta = 4\left(-\frac{V_1 s}{5}\right)$$

$$\therefore V_2 = (0.8s + 1)V_1$$

Simplifying:

$$V_o(2s + 1) - V_1(1.6s^2 + 2s + 1) = 500$$

$$-V_o(2s + 1) - V_1(11.6s^2 + 12s + 1) = 0$$

$$\Delta = \begin{vmatrix} 2s + 1 & -(1.6s^2 + 2s + 1) \\ -(2s + 1) & (11.6s^2 + 12s + 1) \end{vmatrix} = 20(s^2 + 1.5s + 0.5)$$

$$N_o = \begin{vmatrix} 500 & -(1.6s^2 + 2s + 1) \\ 0 & (11.6s^2 + 12s + 1) \end{vmatrix} = 500(11.6s^2 + 12s + 1)$$

$$V_o = \frac{N_o}{\Delta} = \frac{25(11.6s^2 + 12s + 1)}{s(s + 0.5)(s + 1)}$$


[b] $v_o(0^+) = \lim_{s \rightarrow \infty} sV_o = 25(11.6) = 290 \text{ V}$

$$v_o(\infty) = \lim_{s \rightarrow 0} sV_o = \frac{25}{0.5} = 50 \text{ V}$$

[c] At $t = 0^+$ the circuit is

Prob 13.30 (Cont'd)

[c] At $t = 0^+$ the circuit is

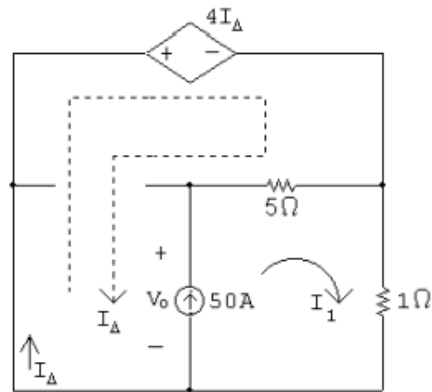

$$4I_{\Delta} + 1I_1 = 0; \quad I_1 - I_{\Delta} = 50$$


$$\therefore 4I_{\Delta} + 50 + I_{\Delta} = 0; \quad 5I_{\Delta} = -50$$

$$\therefore I_{\Delta} = I_o(0^+) = -10\text{ A}$$

$$\text{Also } I_1 = 50 - 10 = 40\text{ A}$$

$$V_o(0^+) = 5(I_1 - I_{\Delta}) + 1I_1 = 6I_1 - 5I_{\Delta} = 240 - 5(-10) = 290\text{ V (checks)}$$

At $t = \infty$ the circuit is

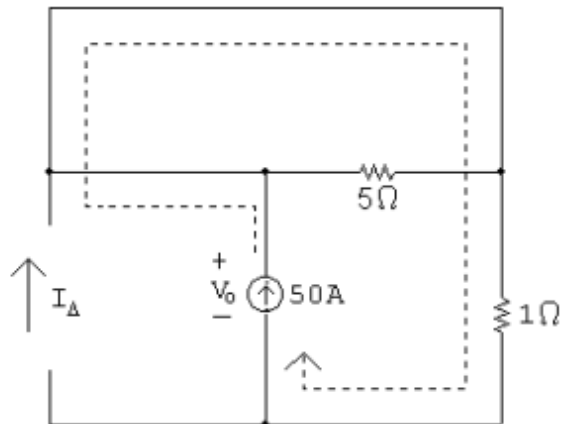

$$V_o(\infty) = 50(1) = 50\text{ V (checks)}$$

Prob 13.30 (Cont'd)

$$[d] V_o = \frac{25(11.6s^2 + 12s + 1)}{s(s + 0.5)(s + 1)} = \frac{K_1}{s} + \frac{K_2}{s + 0.5} + \frac{K_3}{s + 1}$$

$$K_1 = \frac{25}{(0.5)(1)} = 50; \quad K_2 = \frac{-52.5}{(-0.5)(0.5)} = 210$$

$$K_3 = \frac{15}{(-1)(-0.5)} = 30$$

$$V_o = \frac{50}{s} + \frac{210}{s + 0.5} + \frac{30}{s + 1}$$

$$v_o(t) = (50 + 210e^{-0.5t} + 30e^{-t})u(t) \text{ V}$$

$$v_o(\infty) = 50 \text{ V (checks)}$$

$$v_o(0^+) = 50 + 210 + 30 = 290 \text{ V (checks)}$$

Prob 13.54

$$P\ 13.54\ [a]\ Z_i = 1000 + \frac{5 \times 10^6}{s} = \frac{1000(s + 5000)}{s}$$

$$Z_f = \frac{40 \times 10^6}{s} \parallel 40,000 = \frac{40 \times 10^6}{s + 1000}$$

$$H(s) = -\frac{Z_f}{Z_i} = \frac{-40 \times 10^6 / (s + 1000)}{1000(s + 5000) / s} = \frac{-40,000s}{(s + 1000)(s + 5000)}$$

[b] Zero at $z_1 = 0$; Poles at $-p_1 = -1000$ rad/s and $-p_2 = -5000$ rad/s

Prob 13.64

P 13.64 [a] From Problem 13.50(a)

$$H(s) = \frac{250}{s + 250}$$

$$h(\lambda) = 250e^{-250\lambda}$$


$0 \leq t \leq 4$ ms:

$$v_o = \int_0^t 16(250)e^{-250\lambda} d\lambda = 16(1 - e^{-250t})\text{ V}$$

4 ms $\leq t \leq \infty$:

$$v_o = \int_{t-0.004}^t 16(250)e^{-250\lambda} d\lambda = 16(e - 1)e^{-250t}\text{ V}$$

[b]

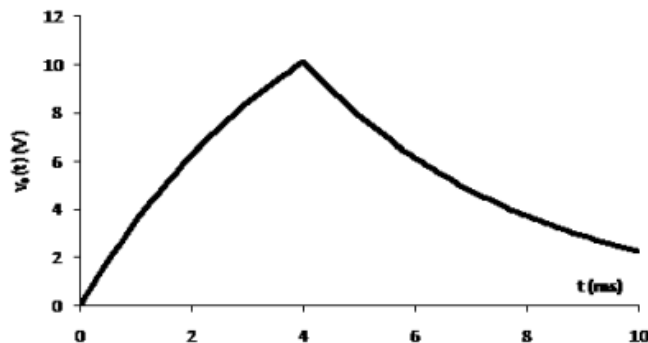

Prob 14.4

$$\text{P 14.4 [a]} \quad \omega_c = \frac{1}{RC} = \frac{1}{(10^3)(100 \times 10^{-9})} = 10 \text{ krad/s}$$

$$f_c = \frac{\omega_c}{2\pi} = 1591.55 \text{ Hz}$$

$$\text{[b]} \quad H(j\omega) = \frac{\omega_c}{s + \omega_c} = \frac{10,000}{s + 10,000}$$

$$H(j\omega) = \frac{10,000}{10,000 + j\omega}$$

$$H(j\omega_c) = \frac{10,000}{10,000 + j10,000} = 0.7071 / \underline{-45^\circ}$$

$$H(j0.1\omega_c) = \frac{10,000}{10,000 + j1000} = 0.9950 / \underline{-5.71^\circ}$$

$$H(j10\omega_c) = \frac{10,000}{10,000 + j100,000} = 0.0995 / \underline{-84.29^\circ}$$

$$\text{[c]} \quad v_o(t)|_{\omega_c} = 200(0.7071) \cos(10,000t - 45^\circ)$$

$$= 141.42 \cos(10,000t - 45^\circ) \text{ mV}$$

$$v_o(t)|_{0.1\omega_c} = 200(0.9950) \cos(1000t - 5.71^\circ)$$

$$= 199.01 \cos(1000t - 5.71^\circ) \text{ mV}$$

$$v_o(t)|_{10\omega_c} = 200(0.0995) \cos(100,000t - 84.29^\circ)$$

$$= 19.90 \cos(100,000t - 84.29^\circ) \text{ mV}$$

Prob 14.32

$$\text{P 14.32 [a]} \quad \omega_o^2 = \frac{1}{LC} = \frac{1}{(5 \times 10^{-3})(200 \times 10^{-12})} = 10^{12}$$

$$\omega_o = 1 \text{ Mrad/s}$$

$$\text{[b]} \quad \beta = \frac{R + R_L}{R_L} \cdot \frac{1}{RC} = \left(\frac{500 \times 10^3}{400 \times 10^3} \right) \left(\frac{1}{(100 \times 10^3)(200 \times 10^{-12})} \right) = 62.5 \text{ krad/s}$$

$$\text{[c]} \quad Q = \frac{\omega_o}{\beta} = \frac{10^6}{62.5 \times 10^3} = 16$$

$$\text{[d]} \quad H(j\omega_o) = \frac{R_L}{R + R_L} = 0.8 \angle 0^\circ$$


$$\therefore v_o(t) = 250(0.8) \cos(10^6 t) = 200 \cos 10^6 t \text{ mV}$$

$$\text{[e]} \quad \beta = \left(1 + \frac{R}{R_L} \right) \frac{1}{RC} = \left(1 + \frac{100}{R_L} \right) (50 \times 10^3) \text{ rad/s}$$

$$\omega_o = 10^6 \text{ rad/s}$$

$$Q = \frac{\omega_o}{\beta} = \frac{20}{1 + (100/R_L)} \quad \text{where } R_L \text{ is in kilohms}$$

[f]

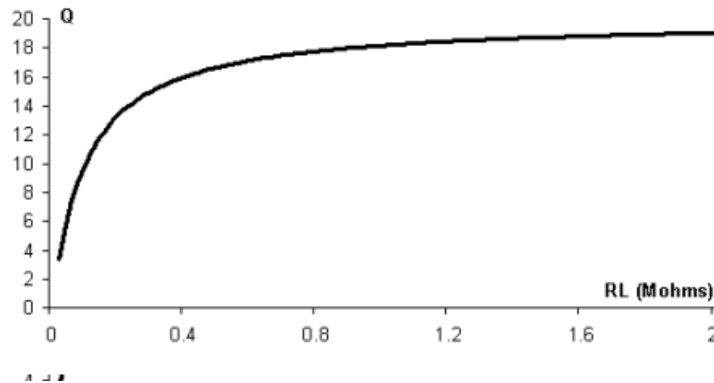

Prob 14.35

$$\text{P 14.35 [a]} \quad \omega_o^2 = \frac{1}{LC} = \frac{1}{(50 \times 10^{-6})(20 \times 10^{-9})} = 10^{12}$$

$$\therefore \omega_o = 1 \text{ Mrad/s}$$

$$\text{[b]} \quad f_o = \frac{\omega_o}{2\pi} = 159.15 \text{ kHz}$$

$$\text{[c]} \quad Q = \omega_o RC = (10^6)(750)(20 \times 10^{-9}) = 15$$

$$\begin{aligned} \text{[d]} \quad \omega_{c1} &= \omega_o \left[-\frac{1}{2Q} + \sqrt{1 + \left(\frac{1}{2Q}\right)^2} \right] = 10^6 \left[-\frac{1}{30} + \sqrt{1 + \frac{1}{900}} \right] \\ &= 967.22 \text{ krad/s} \end{aligned}$$

$$\text{[e]} \quad f_{c1} = \frac{\omega_{c1}}{2\pi} = 153.94 \text{ kHz}$$

$$\begin{aligned} \text{[f]} \quad \omega_{c2} &= \omega_o \left[\frac{1}{2Q} + \sqrt{1 + \left(\frac{1}{2Q}\right)^2} \right] = 10^6 \left[\frac{1}{30} + \sqrt{1 + \frac{1}{900}} \right] \\ &= 1.03 \text{ Mrad/s} \end{aligned}$$


$$\text{[g]} \quad f_{c2} = \frac{\omega_{c2}}{2\pi} = 164.55 \text{ kHz}$$

$$\text{[h]} \quad \beta = f_{c2} - f_{c1} = 10.61 \text{ kHz}$$

Prob 15.4

P 15.4 [a] $\omega_c = \frac{1}{R_2 C}$ so $R_2 = \frac{1}{\omega_c C} = \frac{1}{2\pi(2500)(10 \times 10^{-9})} = 6366 \Omega$
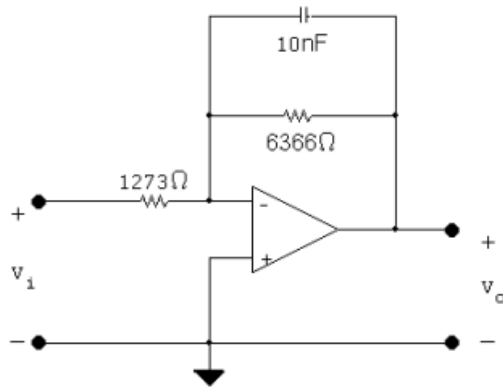
$$K = \frac{R_2}{R_1} \text{ so } R_1 = \frac{R_2}{K} = \frac{6366}{5} = 1273 \Omega$$



[b] Both the cutoff frequency and the passband gain are changed.

Prob 15.25

P 15.25 From the solution to Problem 14.35, $\omega_o = 10^6$ rad/s and $\beta = 2\pi(10.61)$ krad/s. Calculate the scale factors:

$$k_f = \frac{\omega'_o}{\omega_o} = \frac{50 \times 10^3}{10^6} = 0.05$$

$$k_m = \frac{k_f L'}{L} = \frac{0.05(200 \times 10^{-6})}{50 \times 10^{-6}} = 0.2$$

Thus,

$$R' = k_m R = (0.2)(750) = 150 \Omega \qquad C' = \frac{C}{k_m k_f} = \frac{20 \times 10^{-9}}{(0.2)(0.05)} = 2 \mu\text{F}$$

Calculate the bandwidth:

$$\beta' = k_f \beta = (0.05)[2\pi(10.6 \times 10^3)] = 3330 \text{ rad/s}$$

To check, calculate the quality factor:

$$Q = \frac{\omega_o}{\beta} = \frac{10^6}{2\pi(10.61 \times 10^3)} = 15$$

$$Q' = \frac{\omega'_o}{\beta'} = \frac{50 \times 10^3}{3330} = 15 \text{ (checks)}$$

Prob 15.60

P 15.60 [a] $\omega_o = 2000\pi$ rad/s

$$\therefore k_f = \frac{\omega'_o}{\omega_o} = 2000\pi$$

$$k_m = \frac{C}{C'k_f} = \frac{1}{(15 \times 10^{-9})(2000\pi)} = \frac{10^5}{3\pi}$$

$$R' = k_m R = \frac{10^5}{3\pi}(1) = 10,610 \Omega \quad \text{so} \quad R'/2 = 5305 \Omega$$


$$\sigma = 1 - \frac{1}{4Q} = 1 - \frac{1}{4(20)} = 0.9875$$

$$\sigma R' = 10,478 \Omega; \quad (1 - \sigma)R' = 133 \Omega$$

$$C' = 15 \text{ nF}$$

$$2C' = 30 \text{ nF}$$

[b]

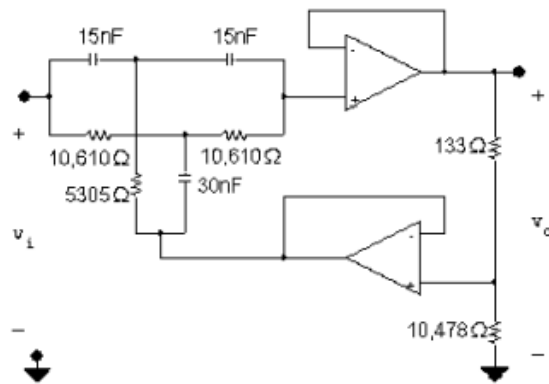

[c] $k_f = 2000\pi$

$$\begin{aligned} H(s) &= \frac{(s/2000\pi)^2 + 1}{(s/2000\pi)^2 + \frac{1}{20}(s/2000\pi) + 1} \\ &= \frac{s^2 + 4 \times 10^6 \pi^2}{s^2 + 100\pi s + 4 \times 10^6 \pi^2} \end{aligned}$$